

# Digital Integrated Circuit

## Lecture 8 MOS Transistor Theory

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**

# Lecture 7

- Nonideal IV
  - Mobility degradation due to the vertical electric field
  - Velocity saturation

## 2.4 Nonideal IV

## 2.4. Nonideal IV (7)

- Velocity saturation
  - Saturation velocity (Canali model)
  - Electrons:  $1.07 \times 10^7$  cm/sec
  - Holes:  $8.37 \times 10^6$  cm/sec
  - A simple model

$$v = \begin{cases} \frac{\mu_{\text{eff}} E}{1 + \frac{E}{E_c}} & E < E_c \\ v_{\text{sat}} & E \geq E_c \end{cases}$$

$$E_c = \frac{2v_{\text{sat}}}{\mu_{\text{eff}}}$$

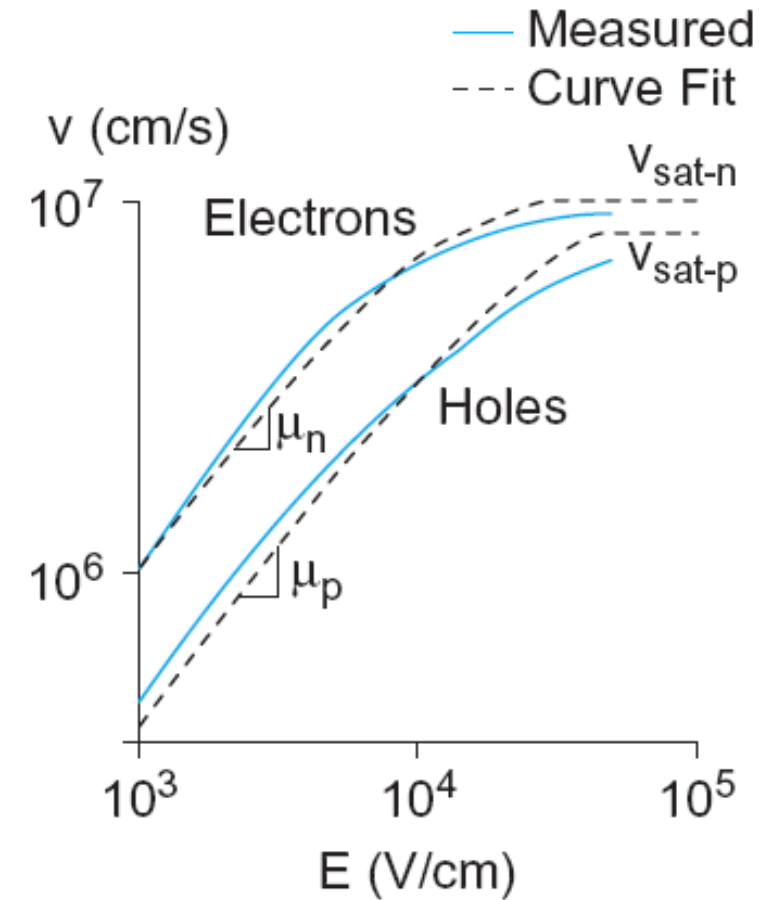


Fig. 2.15

## 2.4. Nonideal IV (8)

- When the electric field is lower than  $E_c$ ,

$$E = \frac{I_d}{\mu_n C_{OX} W (V_g - V_t - V_c) - \frac{I_d}{E_c}} = \frac{dV_c}{dx}$$

- (Note that the sign is not correct but understood.)
- Then, the integration gives

$$\begin{aligned} LI_d &= \int_{V_s}^{V_d} \left[ \mu_n C_{OX} W (V_g - V_t - V_c) - \frac{I_d}{E_c} \right] dV_c \\ &= \mu_n C_{OX} W \left[ (V_g - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right] - \frac{I_d}{E_c} V_{ds} \end{aligned}$$

## 2.4. Nonideal IV (9)

- Drain current with the velocity saturation

$$I_d = \frac{1}{L + \frac{V_{ds}}{E_c}} \mu_n C_{OX} W \left[ (V_g - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$$

– With  $V_c = E_c L$ ,

$$I_d = \frac{1}{1 + \frac{V_{ds}}{V_c}} \mu_n C_{OX} \frac{W}{L} \left[ (V_g - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$$

– The factor,  $\frac{1}{1 + \frac{V_{ds}}{V_c}}$ , describes the velocity saturation.

– Then, when do we have the saturation?

## 2.4. Nonideal IV (10)

- Condition for saturation,  $E = E_c @ x = L$ 
  - In this case,  $V_d = V_{dsat}$  and  $I_d = I_{dsat}$

$$E_c = \frac{I_{dsat}}{\mu_n C_{OX} W (V_g - V_t - V_{dsat}) - \frac{I_{dsat}}{E_c}}$$

- The saturation current becomes

$$I_{dsat} = \frac{1}{2} \mu_n C_{OX} W (V_g - V_t - V_{dsat}) E_c$$

- What is  $V_{dsat}$ ?



## 2.4. Nonideal IV (11)

- Equating two expressions,

$$I_{dsat} = \frac{1}{2} \mu_n C_{OX} W (V_g - V_t - V_{dsat}) E_c$$
$$I_{dsat} = \frac{1}{1 + \frac{V_{dsat}}{V_c}} \mu_n C_{OX} \frac{W}{L} \left[ (V_g - V_t) V_{dsat} - \frac{1}{2} V_{dsat}^2 \right]$$

- With the gate overdrive voltage,  $V_{GT} \equiv V_g - V_t$ , we can find

$$V_{dsat} = \frac{V_{GT} V_c}{V_{GT} + V_c}$$
$$I_{dsat} = C_{OX} W \frac{V_{GT}^2}{V_{GT} + V_c} v_{sat}$$

- Two extreme cases,  $V_{GT} \ll V_c$  and  $V_{GT} \gg V_c$

# Homework#2

- Due: AM08:00, September 26
- Problem#1
  - Compare three modes for the velocity saturation:
  - 1) The one studied in this lecture. (For this model,  $E_c$  is 22 kV/cm)
  - 2)  $v = \frac{\mu_{eff} E}{\sqrt{1 + \left(\frac{E}{E_c}\right)^2}}$
  - 3)  $v = \frac{\mu_{eff} E}{1 + \frac{E}{E_c}}$  for any  $E$  value
  - Draw the velocity-field graph in the semi-logarithmic scale.  $\mu_{eff}$  is 710 cm<sup>2</sup>/V sec.  $E_c$  is 11 kV/cm for 2) and 3). The electric field varies from 100 V/cm to 100 kV/cm.

# Homework#2

- Problem#2

- Draw the output characteristics of an NMOSFET, by using two IV models. Compare them.
- 1) Long-channel IV
- 2) The one studied in this lecture.
- Parameters are:  $W$  is 100  $\mu\text{m}$ .  $L$  is 1  $\mu\text{m}$ .  $t_{ox}$  is 25 nm. The effective mobility is assumed to be a constant of 500  $\text{cm}^2/\text{V sec}$ , for simplicity.  $E_c$  is 11 kV/cm. Consider five values of  $V_{GT}$ : 0.5 V, 1.0 V, 1.5 V, 2.0 V, and 2.5 V. Increase the drain voltage up to 3.0 V.

## 2.4. Nonideal IV (12)

- Threshold voltage (Body effect)

- It is given by

$$V_t = \frac{\sqrt{2\epsilon_{si}qN_A}}{C_{ox}} \sqrt{\phi_s + V_{sb}} + V_{FB} + \phi_s$$

$$\phi_s = 2v_T \log \frac{N_A}{n_i}$$

- At zero  $V_{sb}$ ,

$$V_{t0} = \gamma \sqrt{\phi_s + V_{sb}} + V_{FB} + \phi_s$$

- Therefore,

$$V_t = V_{t0} + \gamma (\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s})$$

## 2.4. Nonideal IV (13)

- Leakage
  - Subthreshold slope
  - Drain-induced barrier lowering
  - Gate-induced drain leakage

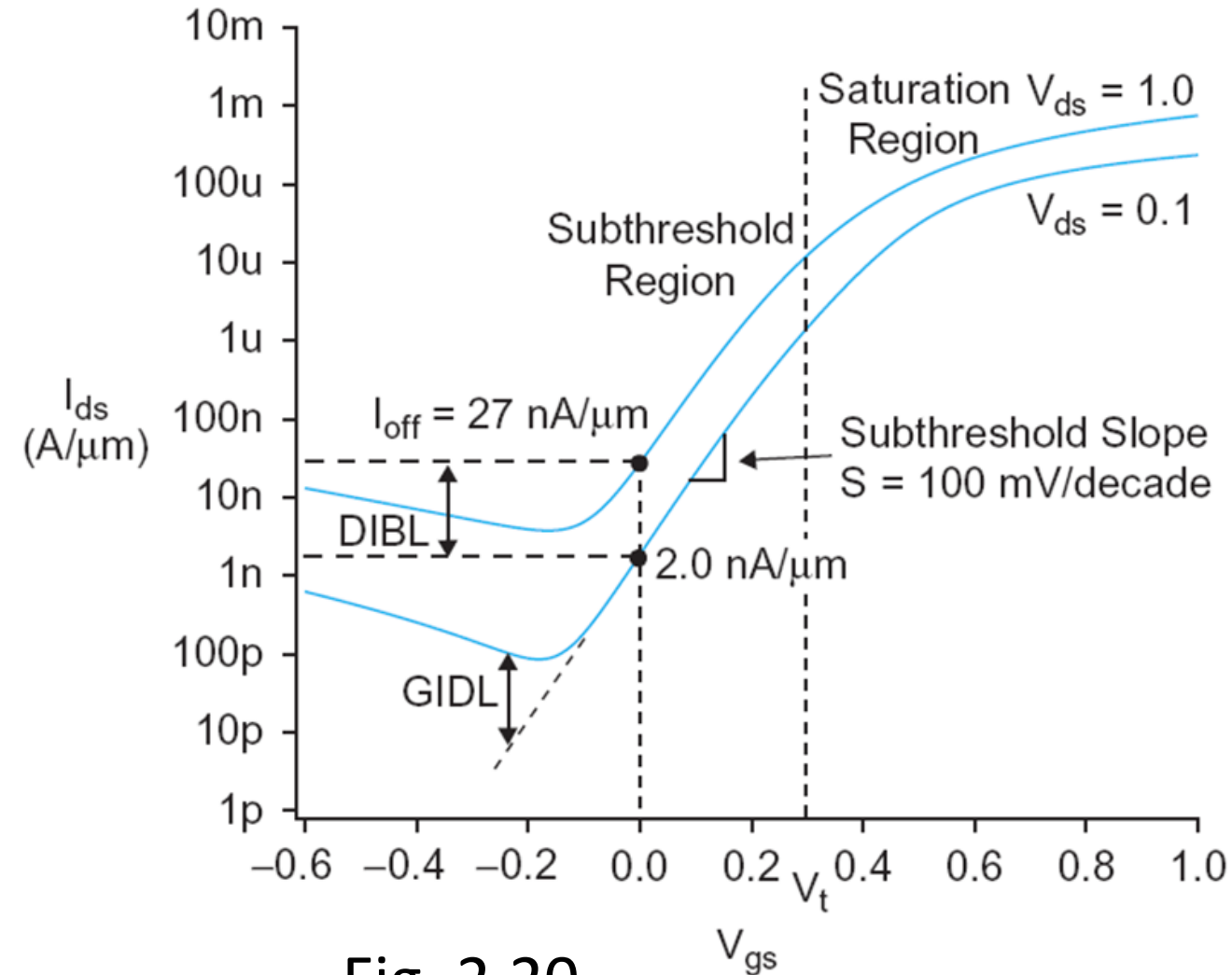


Fig. 2.20

## 2.5 DC Transfer

## 2.5. DC transfer (1)

- A CMOS inverter
  - The transistor is a switch with an infinite off-resistance and a finite on-resistance.


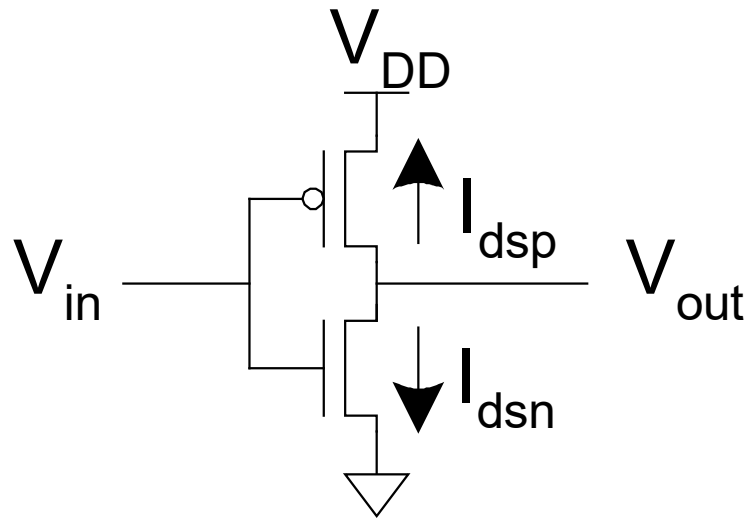


Fig. 2.25

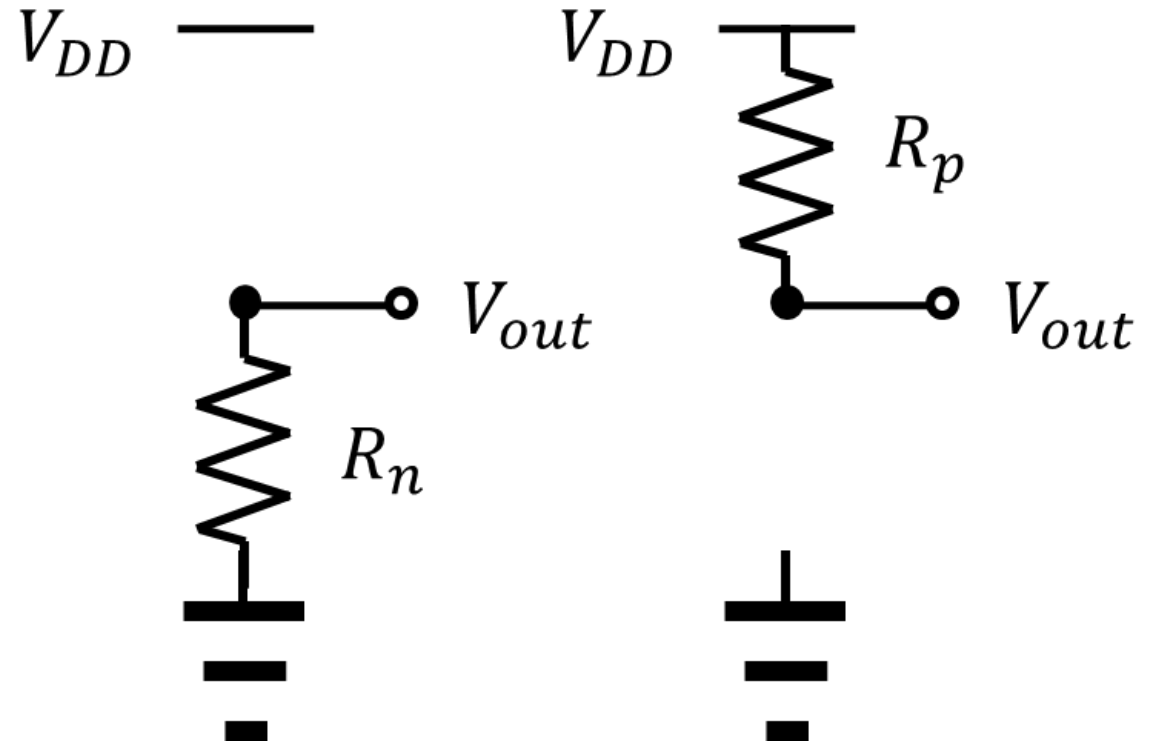

## 2.5. DC transfer (2)

- Important properties (Taken from Rabaey's book)
  - The HIGH and LOW output levels equal  $V_{DD}$  and GND, respectively.
  - The logic levels are not dependent upon the relative device sizes, so that the transistors can be minimum size. (Ratioless)
  - A well-designed CMOS inverter has a low output impedance.
  - The input resistance of the CMOS inverter is extremely high.
  - The absence of current flow between  $V_{DD}$  and GND means that the logic gate does not consume any static power.



## 2.5. DC transfer (3)

- We have five points. Identify the operational modes of transistors.

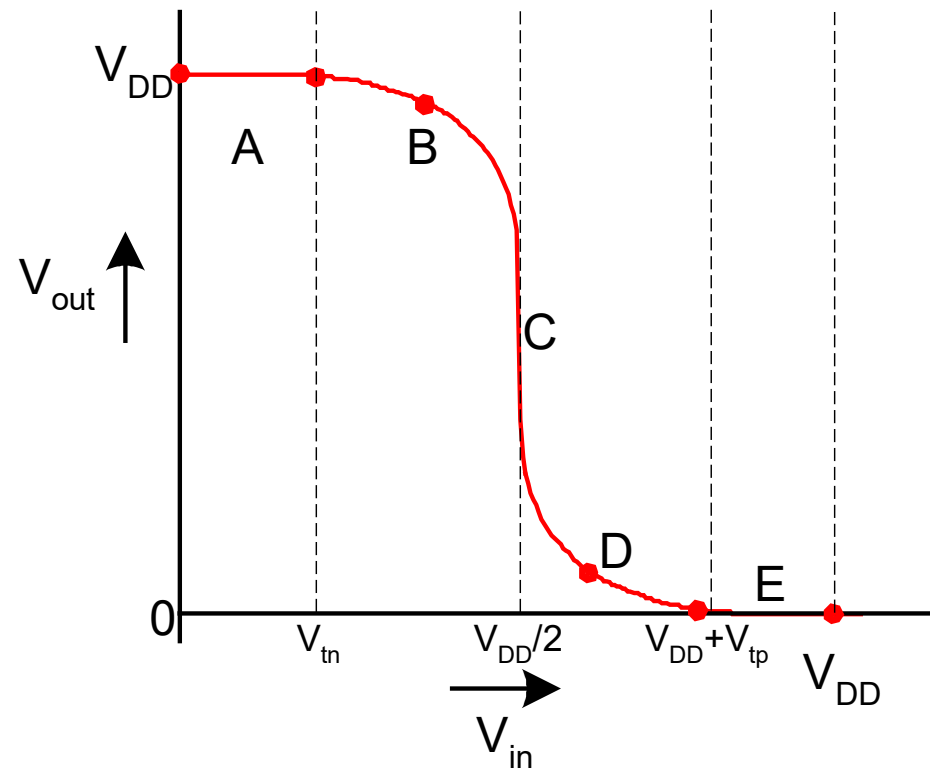


Fig. 2.26(c)

## 2.5. DC transfer (4)

- Input threshold,  $V_{inv}$  (or switching threshold)
  - When  $V_{in} = V_{out} = V_{inv}$
- $\beta$  ( $\frac{W}{L} \mu C_{OX}$ ) ratio
  - HIGH-skewed,  $\frac{\beta_p}{\beta_n} > 1$ , stronger PMOS
  - LOW-skewed,  $\frac{\beta_p}{\beta_n} < 1$ , weaker PMOS

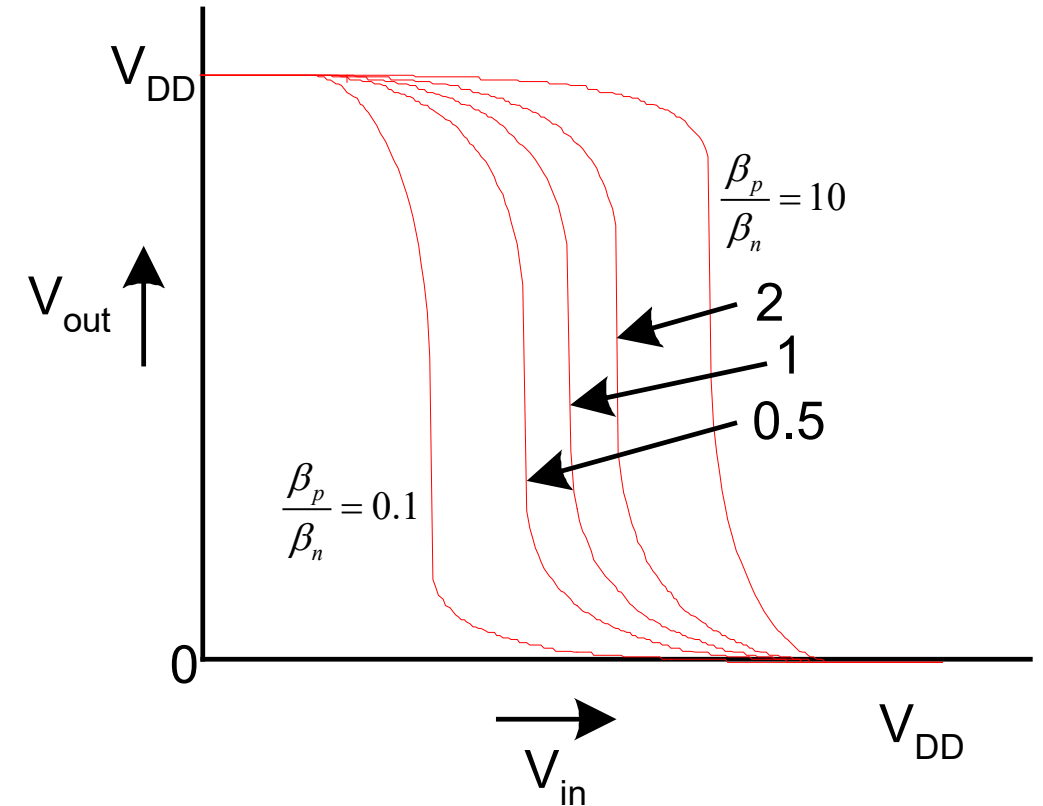


Fig. 2.28

## 2.5. DC transfer (5)

- Quantitative analysis for  $V_{inv}$

- Use the long-channel IV

$$I_{dn} = \frac{\beta_n}{2} (V_{inv} - V_{tn})^2 \text{ and } I_{dp} = -\frac{\beta_p}{2} (V_{inv} - V_{DD} - V_{tp})^2$$

- After manipulation, we have

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$

- (Here,  $r = \frac{\beta_p}{\beta_n}$ )

- For a special case with  $r = 1$ ,  $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$

## 2.5. DC transfer (6)

- Quantitative analysis for  $V_{inv}$  with velocity saturation

- Use the following expressions:

$$I_{dn} = W_n C_{ox} v_{sat-n} (V_{inv} - V_{tn})$$

$$I_{dp} = -W_p C_{ox} v_{sat-p} (V_{inv} - V_{DD} - V_{tp})$$

- After manipulation, we have


$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \frac{1}{r}}{1 + \frac{1}{r}}$$

- (Here,  $r = \frac{W_p v_{sat-p}}{W_n v_{sat-n}}$ )

- For a special case with  $r = 1$ ,  $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$
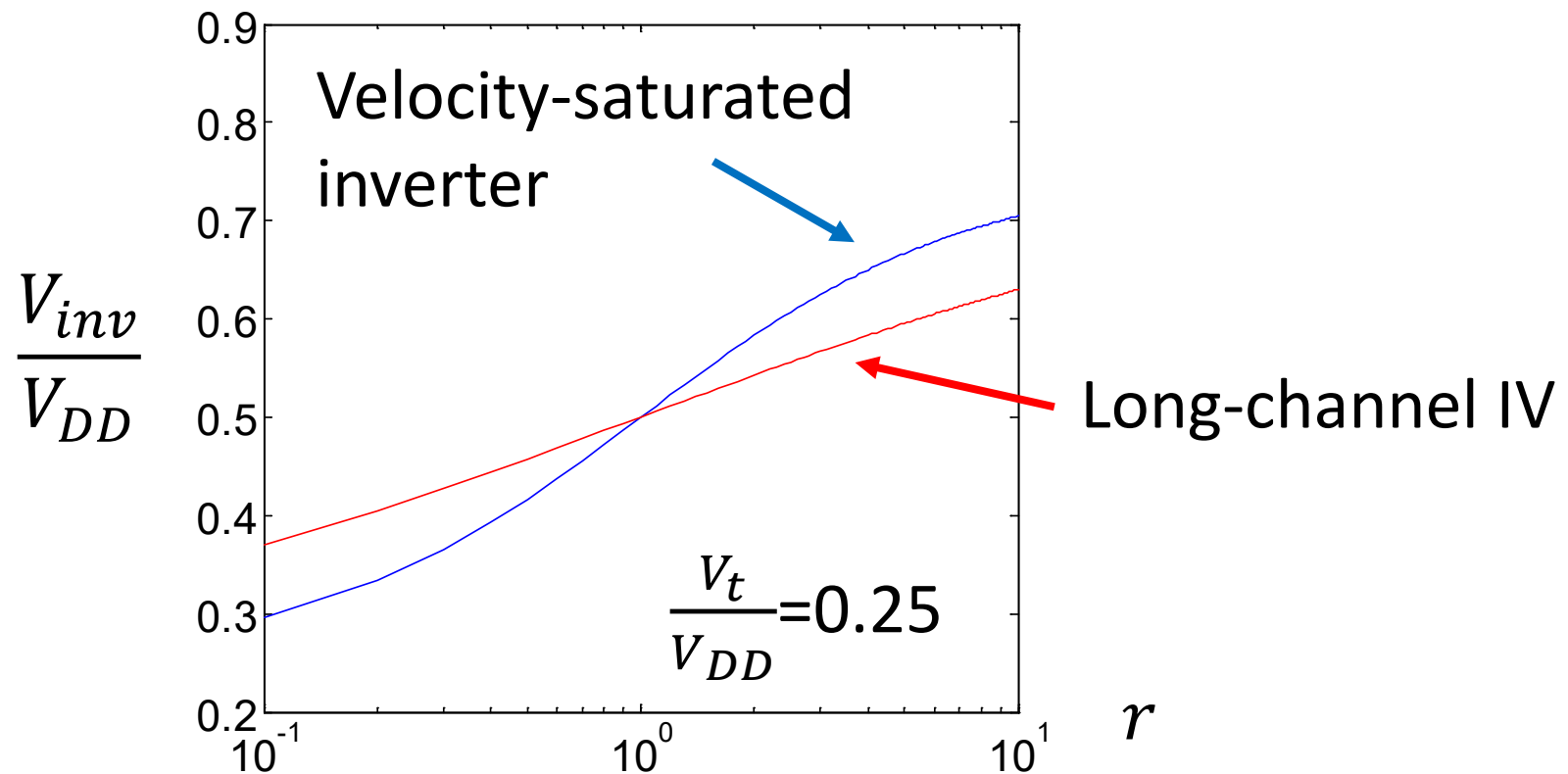
## 2.5. DC transfer (7)

- Compare them.
  - Let's draw  $\frac{V_{inv}}{V_{DD}}$  as a function of  $r$ . Assume that  $V_t = V_{tn} = -V_{tp}$ .



## 2.5. DC transfer (8)

- Width ratio (Velocity-saturated inverter)

- It is found that

$$r = \frac{W_p v_{sat-p}}{W_n v_{sat-n}} = \frac{V_{inv} - V_{tn}}{V_{DD} - V_{tp} - V_{inv}}$$

- The width ratio is given by

$$\frac{W_p}{W_n} = \frac{v_{sat-n}(V_{inv} - V_{tn})}{v_{sat-p}(V_{DD} - V_{tp} - V_{inv})}$$

# Thank you!