

# Digital Integrated Circuit

## Lecture 13 Delay


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**

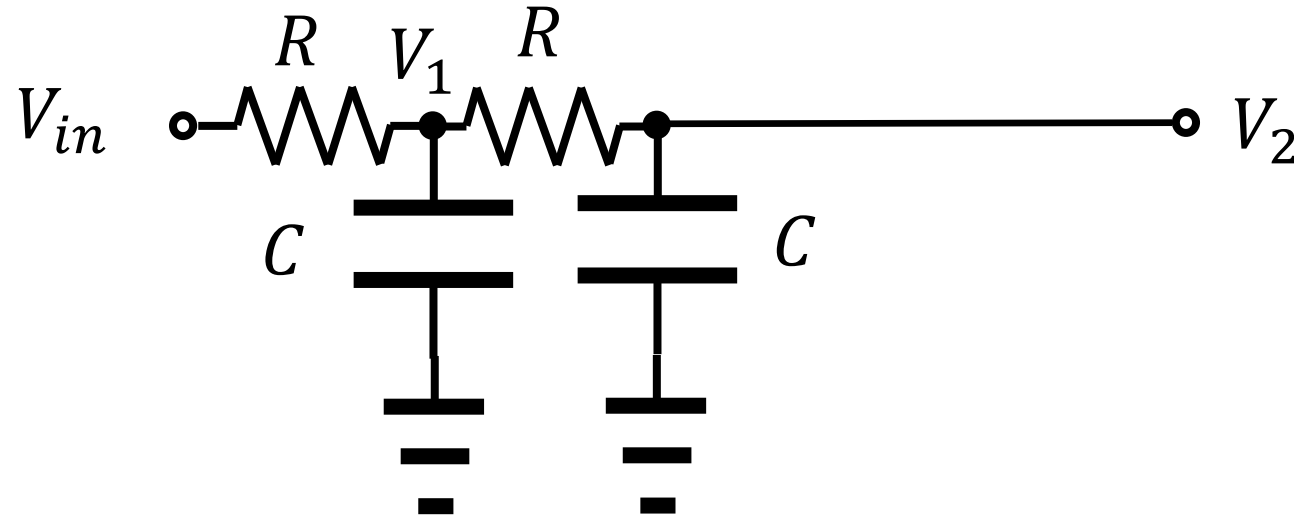
# Lecture 12

- Elmore delay
  - When  $V_2$  is the output voltage,  $\tau = 3RC$ .
  - When  $V_1$  is the output voltage,  $\tau = 2RC$ .



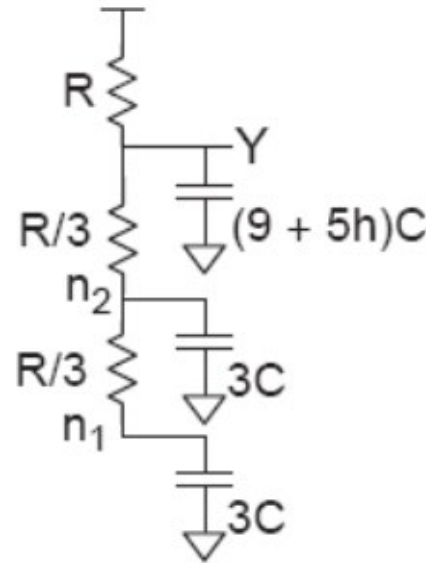
# Lecture 12

- Rising propagation delay
  - In the worst case,  $\tau = (15 + 5h)RC$ .


 
# Lecture 12

- Homework#4
  - Solid (Solution)
  - Dash (Approx.)
  - Red ( $V_2$ )
  - Blue ( $V_1$ )
  - Blue dot (Wrong!)



## 4.3 RC Delay Model

## 4.3. RC delay model (11)

- Delay components
  - *Parastic delay*: Time for a gate to drive its own internal diffusion capacitance
  - *Effort delay*: It depends on the ratio of external load capacitance to input capacitance.
  - The normalized delay,  $d = \frac{t_{pd}}{3RC}$ , can be written as

$$d = \text{parastic delay} + \text{effort delay}$$

## 4.3. RC delay model (12)

- Layout dependence of capacitance
  - A good layout minimizes the diffusion area.

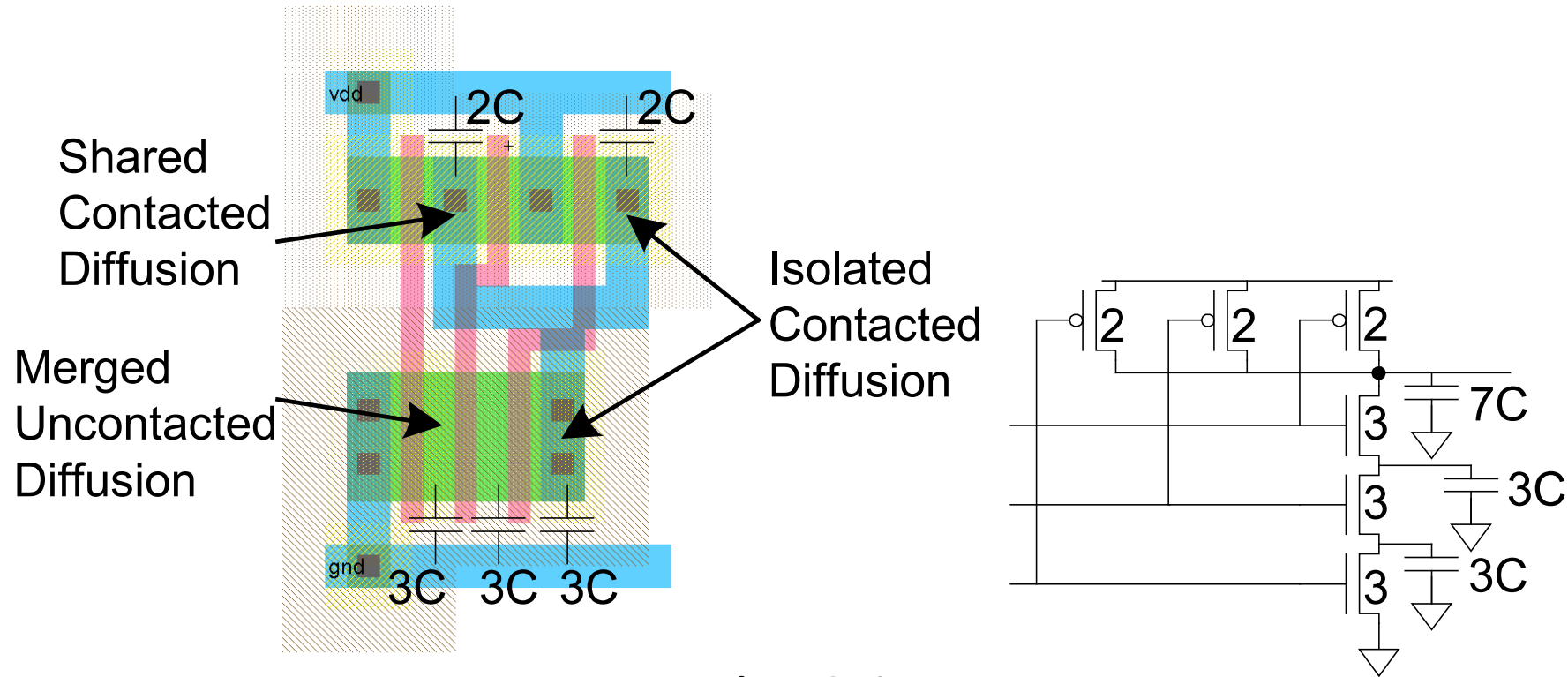


Fig. 4.17



## 4.4 Linear Delay Model

## 4.4. Linear delay model (1)

- Delay in a logic gate
  - Normalized delay

$$d = \frac{t_{pd}}{3RC}$$

- Delay has two components:

$$d = f + p = gh + p$$

- Effort delay:

$$f = gh$$

( $g$  is the logical effort.)

## 4.4. Linear delay model (2)

- Delay in a logic gate


- Fanout (or electrical effort)

$$h = \frac{C_{out}}{C_{in}}$$

(Ratio of output to input capacitance)


- Parasitic delay,  $p$ , represents delay of gate driving no load.

 - $p$  is set by internal parasitic capacitance.



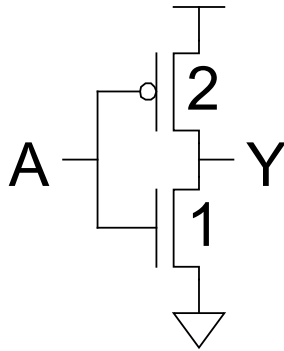
## 4.4. Linear delay model (3)


- Computing logical effort
  - *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*



$$C_{in} = 3$$
$$g = 3/3$$

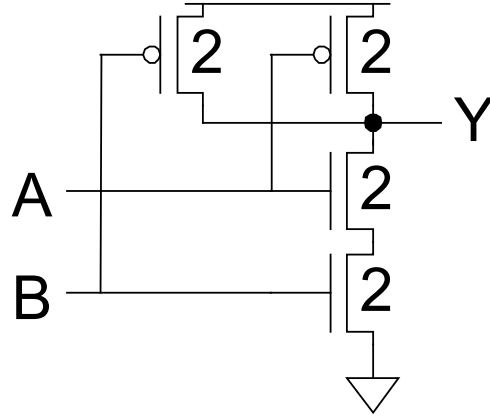

$$C_{in} = 4$$
$$g = 4/3$$

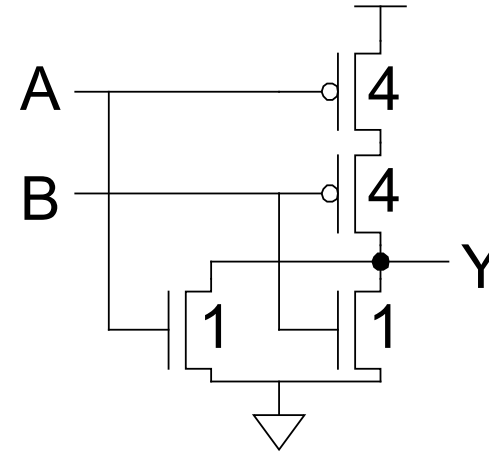

$$C_{in} = 5$$
$$g = 5/3$$

## 4.4. Linear delay model (4)

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	


## 4.4. Linear delay model (5)

- Parasitic delay of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

## 4.4. Linear delay model (6)


- Example 4.10

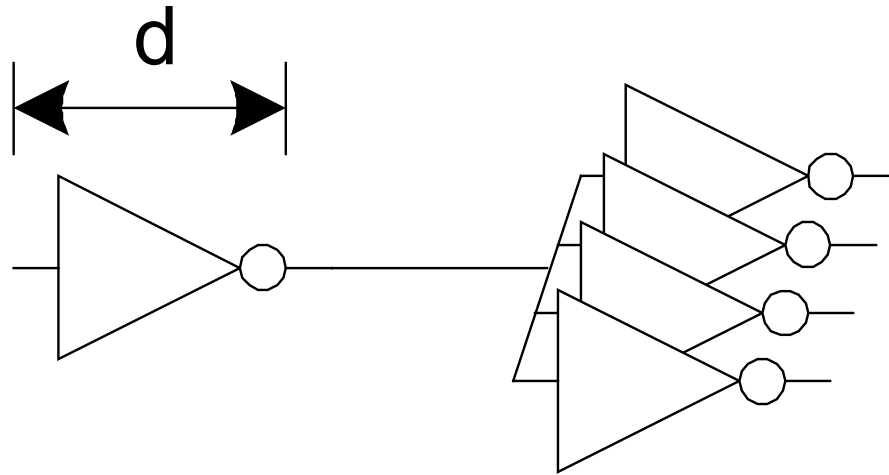

- Logical effort:  $g = 1$
- Electrical effort:  $h = 4$
- Parasitic delay:  $p = 1$
- Stage delay:  $d = 5$
- When  $\tau = 3RC = 3$  ps, the total delay is 15 ps.

## 4.4. Linear delay model (7)

- Example 4.11

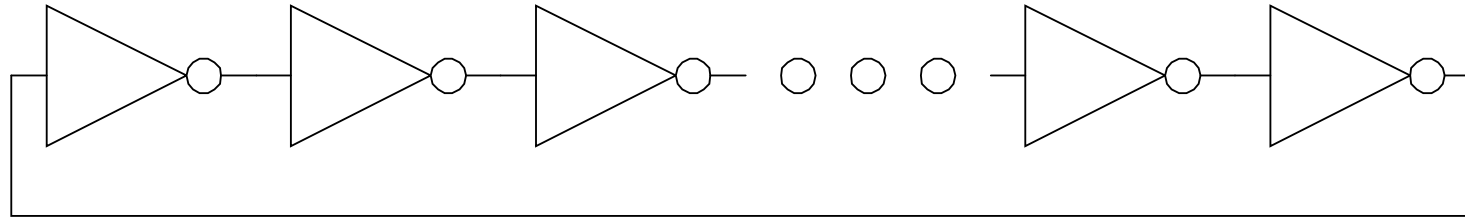

- A ring oscillator with an odd number ( $N$ ) of inverters
- Logical effort:  $g = 1$
- Electrical effort:  $h = 1$
- Parasitic delay:  $p = 1$
- Stage delay:  $d = 2$
- Frequency:  $f_{osc} = \frac{1}{2Nd} = \frac{1}{4Nd}$



# Thank you!