

Digital Integrated Circuit

Lecture 9 MOS Transistor Theory

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Laboratory
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of Previous Lecture

Lecture 8

- Nonideal IV

- Analysis on the velocity saturation

$$V_{dsat} = \frac{V_{GT} V_c}{V_{GT} + V_c}$$

$$V_c = E_c L$$

$$I_{dsat} = C_{OX} W \frac{V_{GT}^2}{V_{GT} + V_c} v_{sat}$$

- Body effect

2.4 Nonideal IV

2.4. Nonideal IV (13)

- Leakage

- Subthreshold slope

$$S = \left[\frac{d(\log_{10} I_d)}{dV_{gs}} \right]^{-1} = n v_T \ln 10$$

- Drain-induced barrier lowering

- Gate-induced drain leakage

I_{ds}
(A/ μ m)

 


Fig. 2.20

2.5 DC Transfer

2.5. DC transfer (1)

- A CMOS inverter
 - The transistor is a switch with an infinite off-resistance and a finite on-resistance.


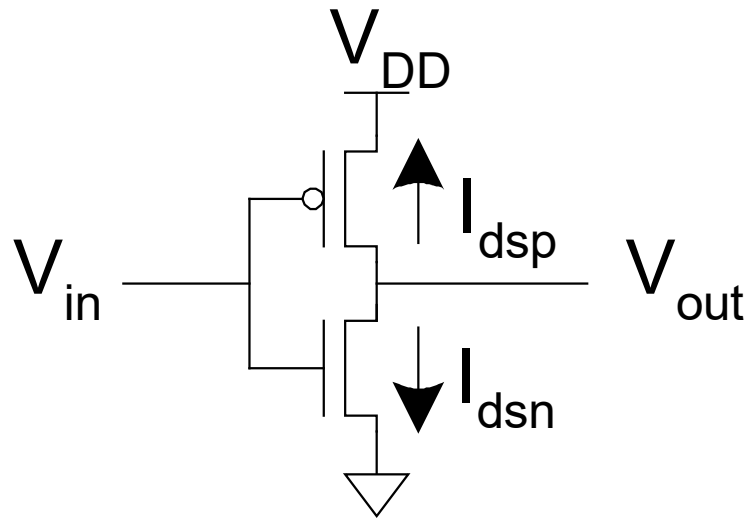


Fig. 2.25

 

2.5. DC transfer (2)

- Important properties (Taken from Rabaey's book)
 - The HIGH and LOW output levels equal V_{DD} and GND, respectively.
 - The logic levels are not dependent upon the relative device sizes, so that the transistors can be minimum size. (Ratioless)
 - A well-designed CMOS inverter has a low output impedance.
 - The input resistance of the CMOS inverter is extremely high.
 - The absence of current flow between V_{DD} and GND means that the logic gate does not consume any static power.

2.5. DC transfer (3)

- We have five points. Identify the operational modes of transistors.

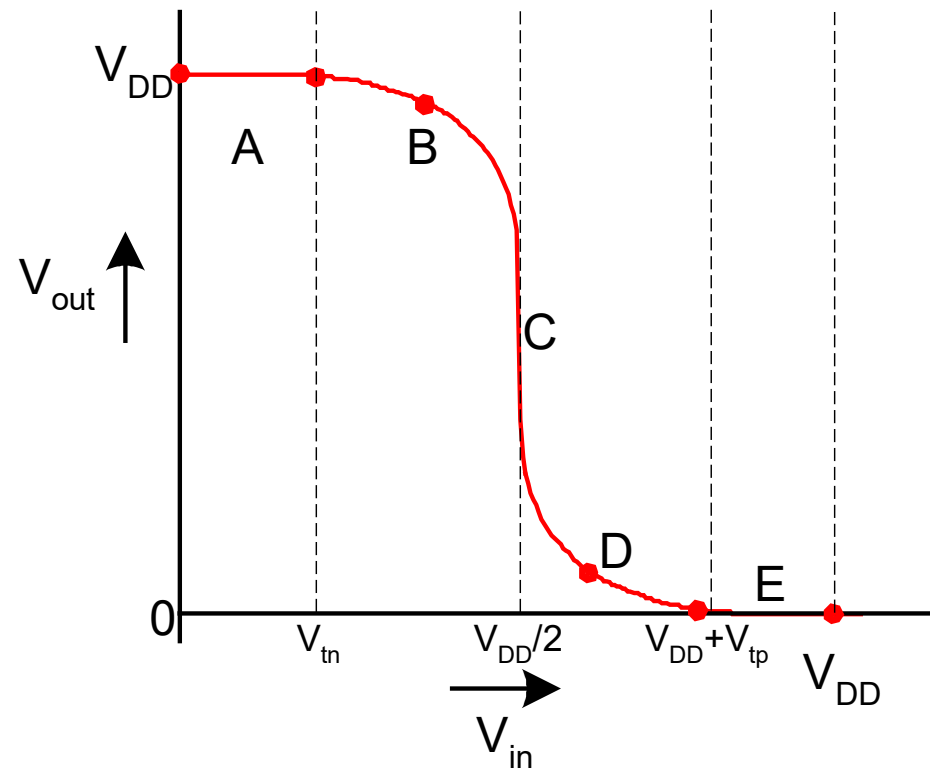


Fig. 2.26(c)

2.5. DC transfer (4)

- Input threshold, V_{inv} (or switching threshold)

- When $V_{in} = V_{out} = V_{inv}$

- β ($\frac{W}{L} \mu C_{OX}$) ratio

- HIGH-skewed, $\frac{\beta_p}{\beta_n} > 1$, stronger PMOS

- LOW-skewed, $\frac{\beta_p}{\beta_n} < 1$, weaker PMOS

 


Fig. 2.28

2.5. DC transfer (5)

- Quantitative analysis for V_{inv}

- Use the long-channel IV

$$I_{dn} = \frac{\beta_n}{2} (V_{inv} - V_{tn})^2 \text{ and } I_{dp} = -\frac{\beta_p}{2} (V_{inv} - V_{DD} - V_{tp})^2$$

- After manipulation, we have

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$

- (Here, $r = \frac{\beta_p}{\beta_n}$)

- For a special case with $r = 1$, $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$

2.5. DC transfer (6)

- Quantitative analysis for V_{inv} with velocity saturation

- Use the following expressions:

$$I_{dn} = W_n C_{ox} v_{sat-n} (V_{inv} - V_{tn})$$

$$I_{dp} = -W_p C_{ox} v_{sat-p} (V_{inv} - V_{DD} - V_{tp})$$

- After manipulation, we have


$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \frac{1}{r}}{1 + \frac{1}{r}}$$

- (Here, $r = \frac{W_p v_{sat-p}}{W_n v_{sat-n}}$)

- For a special case with $r = 1$, $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$

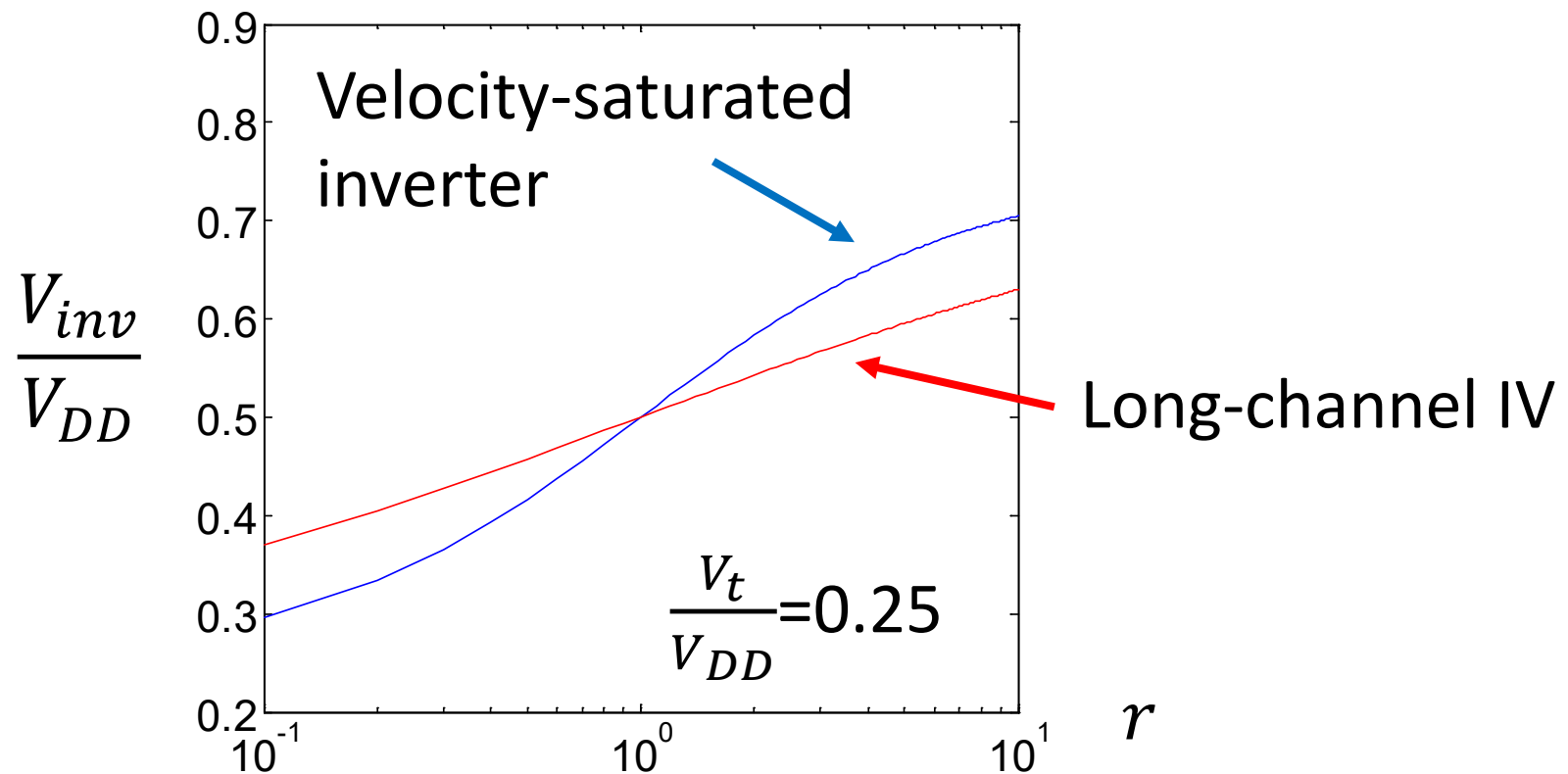2.5. DC transfer (7)

- Compare them.
 - Let's draw $\frac{V_{inv}}{V_{DD}}$ as a function of r . Assume that $V_t = V_{tn} = -V_{tp}$.



2.5. DC transfer (8)

- Width ratio (Velocity-saturated inverter)

- It is found that

$$r = \frac{W_p v_{sat-p}}{W_n v_{sat-n}} = \frac{V_{inv} - V_{tn}}{V_{DD} - V_{tp} - V_{inv}}$$

- The width ratio is given by

$$\frac{W_p}{W_n} = \frac{v_{sat-n}(V_{inv} - V_{tn})}{v_{sat-p}(V_{DD} - V_{tp} - V_{inv})}$$

2.5. DC transfer (9)

- Noise margin

- Two unity gain points
- Input voltage is V_{IL} .
- Input voltage is V_{IH} .

– In this case,

$$NL_L = V_{IL}$$

$$NL_H = V_{DD} - V_{IH}$$

 


Fig. 2.30

Homework#3

- Due: AM08:00, October 5
- Problem#1
 - Calculate V_{IL} with the ideal IV characteristics. It can be found from a condition of $\frac{dV_{out}}{dV_{in}} = -1$. Neglect the channel length modulation.
 - Assume $\mu_n C_{OX} \frac{W_n}{L_n} = \mu_p C_{OX} \frac{W_p}{L_p}$ and $V_{tn} = -V_{tp}$ for simplicity.
 - Hint: The NMOSFET is in the saturation mode, while the PMOSFET in the linear mode.

Homework#3

- Problem#2

- Using the solution of Problem#1, calculate V_{IL} when V_{DD} is 1.8 V and V_{tn} is 0.5 V.

Thank you!