

# Digital Integrated Circuit

## Lecture 22 Combinational Circuit Design

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**

# Lecture 21

- SPICE MOSFET modes
  - Level 1
  - Level 3
  - BSIM
  - Neural compact model

# 9.1 Introduction

# 9.1. Introduction (1)

- Combinational circuit
  - Its outputs depend only on the present inputs.
  - Its building blocks are logic gates.
- Sequential circuit (Ch. 10)
  - It has memory.
  - Its building blocks are registers and latches.

# 9.1. Introduction (2)

- Static CMOS gates
  - They use complementary NMOS and PMOS networks to drive 0 and 1 outputs, respectively.
  - It is robust, fast, energy-efficient, and easy to design.
- Other circuit families
  - Ratioed circuits
  - Dynamic circuits
  - Pass-transistor circuits

# 9.1. Introduction (3)

- What makes a circuit fast?

$$t_{pd} \propto \frac{C}{I} \Delta V$$

- We need:
  - Low capacitance ( $C$ )
  - High current ( $I$ )
  - Small swing ( $\Delta V$ )
- NMOS is preferred.
  - Static CMOS has a relatively large logical effort, due to the PMOS transistors.

## **9.2 Circuit Families**




## 9.2. Circuit families (1)

- Consider a multiplexer. ( $D0$ ,  $D1$ , and  $S$ )

- It can be expressed as

$$Y = D0 \cdot \bar{S} + D1 \cdot S$$

 - So, in general, we need a circuit to compute  $F = AB + CD$ .



## 9.2. Circuit families (2)

- Static CMOS
  - DeMorgan's law

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$
$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

– *Bubble pushing*

- Design a circuit to compute  $F = AB + CD$ .

 


Fig. 9.1

 


Fig. 9.2(a)

## 9.2. Circuit families (3)

- Static CMOS

$$F = AB + CD = \overline{\overline{AB} \cdot \overline{CD}}$$

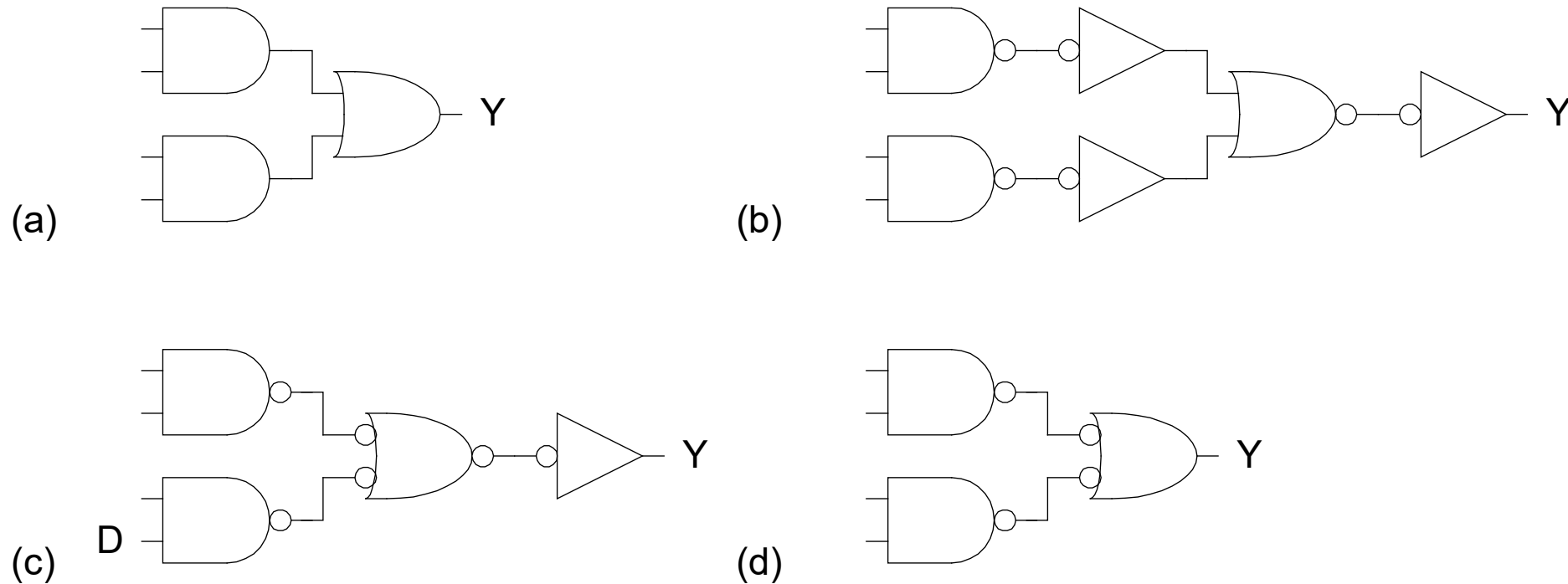


Fig. 9.2

## 9.2. Circuit families (4)

- Using a compound gate (Recall L2.)

$$F = AB + CD = \overline{\overline{AB}} \cdot \overline{\overline{CD}}$$

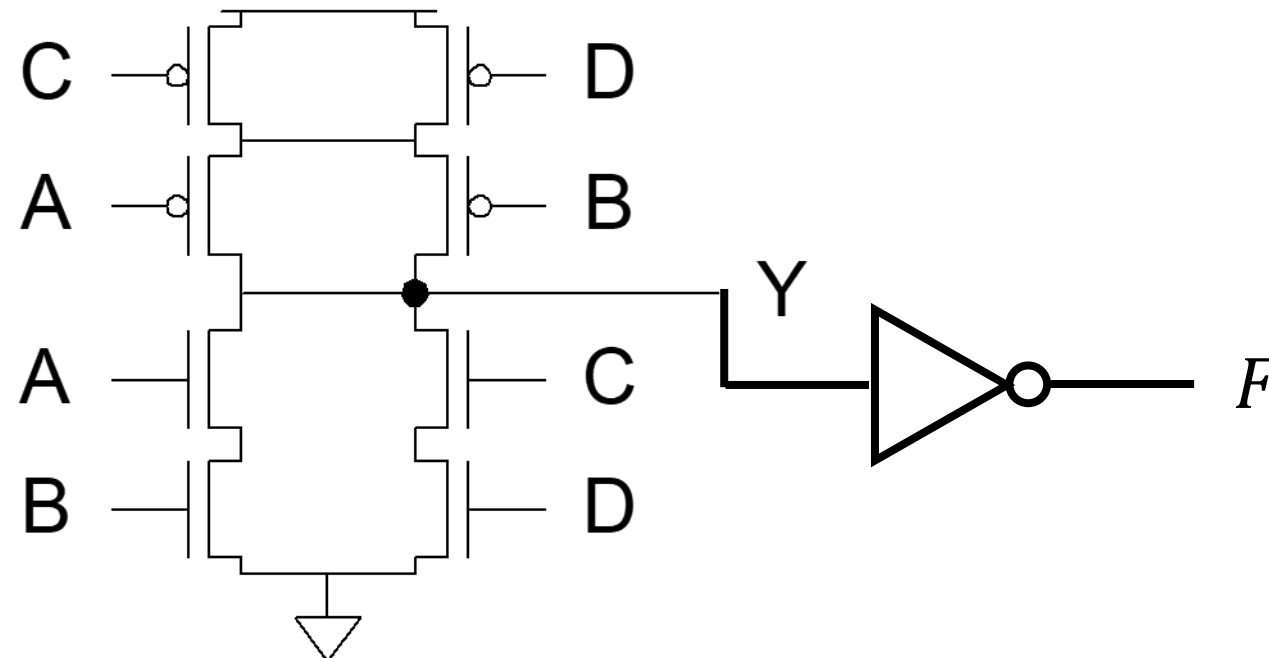
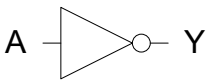
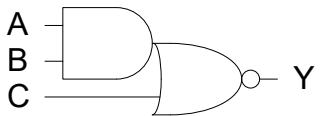
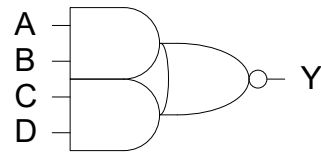
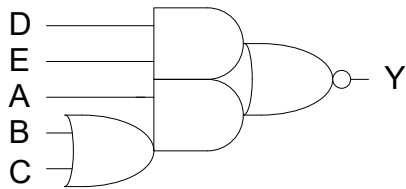
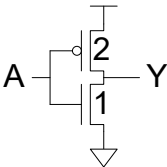
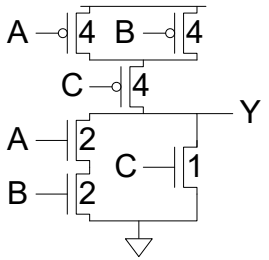
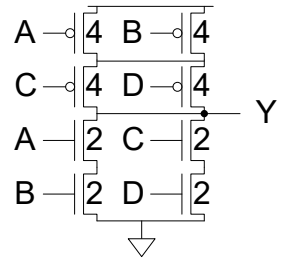
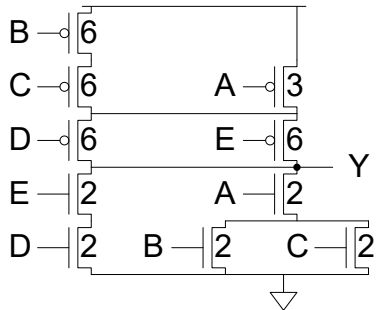


Fig. 1.18(e)

# 9.2. Circuit families (5)

- Logical effort of compound gates

unit inverter	AOI21	AOI22	Complex AOI
$Y = \overline{A}$	$Y = \overline{A \sqcap B + C}$	$Y = \overline{A \sqcap B + C \sqcap D}$	$Y = \overline{A \sqcap (B + C) + D \sqcap E}$
			
			
$g_A = 3/3$ $p = 3/3$	$g_A = 6/3$ $g_B = 6/3$ $g_C = 5/3$ $p = 7/3$	$g_A = 6/3$ $g_B = 6/3$ $g_C = 6/3$ $g_D = 6/3$ $p = 12/3$	$g_A = 5/3$ $g_B = 8/3$ $g_C = 8/3$ $g_D = 8/3$ $g_E = 8/3$ $p = 16/3$

## 9.2. Circuit families (6)

- Input order
  - Consider the falling output transition. (One input holds a stable 1.)
  - If input B rises later, the Elmore delay is  $7RC$ .
  - If input A rises later, the Elmore delay is  $6RC$ .
  - If one signal is known to arrive later than the others, connect the latest signal to the inner input.

 


Fig. 9.6

## 9.2. Circuit families (7)

- Asymmetric gates
  - In this example, suppose that  $A$  is most critical.
  - The circuit is optimized for input-to-output delay at the expense of reset.

 


Fig. 9.7

## 9.2. Circuit families (8)

- Skewed gates
  - Skewed gates favor one edge over another.
  - In this example, suppose that the rising output of the inverter is most critical.
  - Then, we may downsize the noncritical NMOS transistor.
  - Improvement of the critical transition at the expense of noncritical one

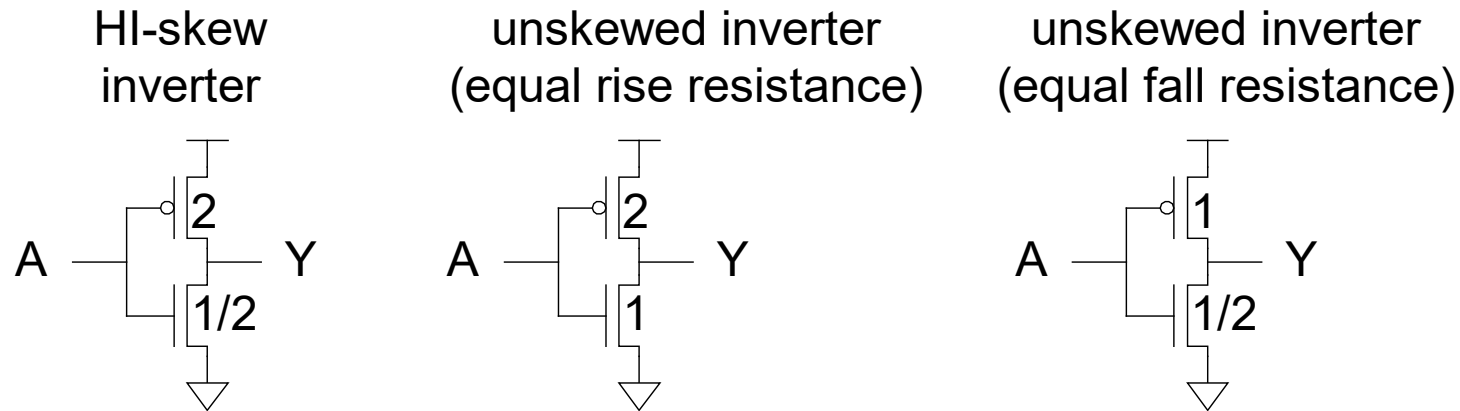


Fig. 9.9



## 9.2. Circuit families (9)



- Best P/N ratio?
  - Assume that the PMOS has  $\mu$  times higher resistance.
  - Then,

$$t_{pdf} = (P + 1)$$

$$t_{pdr} = (P + 1) \frac{\mu}{P}$$

$$t_{pd} = \frac{1}{2} (P + 1) \left( 1 + \frac{\mu}{P} \right)$$

  - When we have  $P = \mu$ ,  $t_{pd}$  becomes  $(\mu + 1)$ .
  - When we have  $P = \sqrt{\mu}$ ,  $t_{pd}$  becomes  $\frac{1}{2} (\sqrt{\mu} + 1)^2$ .
- Area, power, and reliability should be considered.



# Thank you!