

Digital Integrated Circuit

Lecture 2 Introduction

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Laboratory
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of Previous Lecture

Lecture 1

- MOS transistors
 - Its structure: Gate, source, drain and body(/substrate)
 - Controlling the number of charge carriers by using the field effect.
 - (NMOSFET) When $V_{GS} < V_{TH}$, no electron in the channel region
 - (NMOSFET) When $V_{GS} > V_{TH}$, electron density increases linearly with $V_{GS} - V_{TH}$.
 - PMOSFET

1.4 CMOS Logic

1.4. CMOS logic (1)

- CMOS inverter
 - When the input A is 0, the NMOS transistor is OFF and the PMOS transistor is ON.
 - Thus, the output Y is pulled up to 1.

A	$Y = NOT A$
0	1
1	0

 


Fig. 1.11(a)

1.4. CMOS logic (2)

- CMOS NAND

- If either input A or B is 0, at least one of the NMOSFETs will be OFF, breaking the path from Y to GND.

A	B	Y $= A \text{ NAND } B$
0	0	1
0	1	1
1	0	1
1	1	0

 




Fig. 1.12(a)

1.4. CMOS logic (3)

- Complementary CMOS gates
- Pull-down and pull-up networks
 - NMOS pull-down
 - PMOS pull-up

	Pull-up OFF	Pull-up ON
Pull-down OFF	z	1
Pull-down ON	0	Crowbarred (X)

Floating

  

1.4. CMOS logic (4)

- Series and parallel
 - NMOS: 1 = ON
 - PMOS: 0 = ON
 - Series: Both must be ON.
 - Parallel: Either can be ON.
- Conduction complements
 - Pull-up \leftrightarrow pull-down

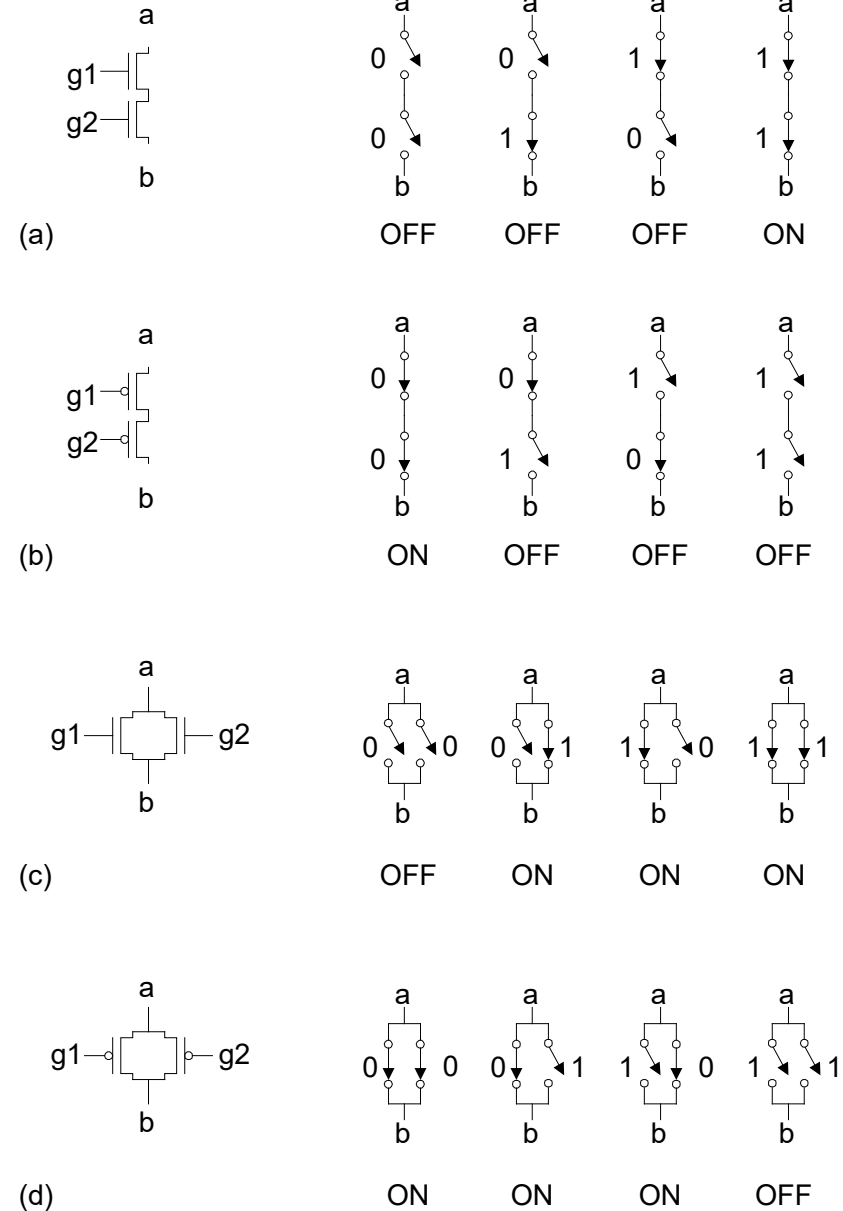


Fig. 1.15

1.4. CMOS logic (5)

- CMOS NOR

 


Fig. 1.16(a)

- Example 1.1
 - Sketch a 3-input CMOS NOR gate.

1.4. CMOS logic (6)

- Compound gates
 - A more complex logic function in a single stage of logic
 - Consider $Y = \overline{(A \cdot B) + (C \cdot D)}$, AND-OR-INVERT-22 (AOI22).

 


Fig. 1.18(e)

1.4. CMOS logic (7)

- Example 1.2

- Sketch a static CMOS gate computing $Y = \overline{(A + B + C) \cdot D}$.

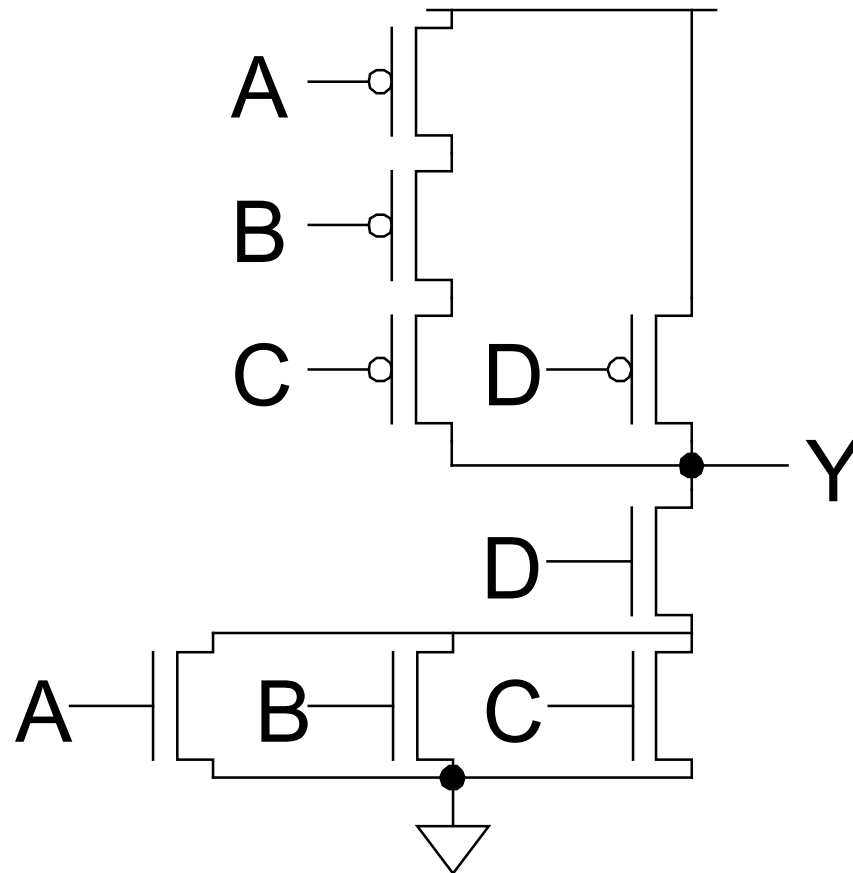


Fig. 1.19

1.4. CMOS logic (8)

- Pass transistors

- Transistors can be used as switches.
- Pass transistors may produce degraded (weak) outputs.


 


Fig. 1.20

 
1.4. CMOS logic (9)

- Transmission gate


- By combining an NMOS and a PMOS transistor in parallel, we obtain a switch that passes both 0 and 1 well. (Transmission gate)



$g = 0, gb = 1$

 


$g = 1, gb = 0$

 

Input

Output

$g = 1, gb = 0$

0 —  — strong 0

$g = 1, gb = 0$

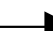
1 —  — strong 1

Fig. 1.21

1.4. CMOS logic (10)

- Tristates (0, 1, and Z)
 - Tristate buffer produces Z when not enabled
 - Transmission gate acts as a tristate buffer.
 - But, it is nonrestoring.

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Truth table of a tristate buffer

 
 


Fig. 1.25

1.4. CMOS logic (11)

- Tristate inverter
 - It produces a restored output.
 - It violates the conduction complements rule. (Why?)

 


Fig. 1.27

1.4. CMOS logic (12)

- Multiplexers (muxes)
 - It chooses the output from several inputs based on a select signal.

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

Truth table of a 2:1 multiplexer

 


Fig. 1.28(b)

1.4. CMOS logic (13)

- Implementation
 - Using transmission gates (nonrestoring)
 - Using tristate inverters (inverting)

 


Fig. 1.28(a)

 


Fig. 1.29(b)

1.4. CMOS logic (14)

- Larger multiplexers
 - Example) 4:1 multiplexer
 - Two levels of 2:1 muxes
 - Or four tristates


 


Fig. 1.30

 

Thank you!