

Digital Integrated Circuit

Lecture 17 Power

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Laboratory
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of Previous Lecture

Lecture 16


- Dynamic power
 - It is dominated by the switching power consumption,
$$P_{switching} = \alpha C V_{DD}^2 f$$
 - Various ways to reduce the switching power

5.3 Static Power

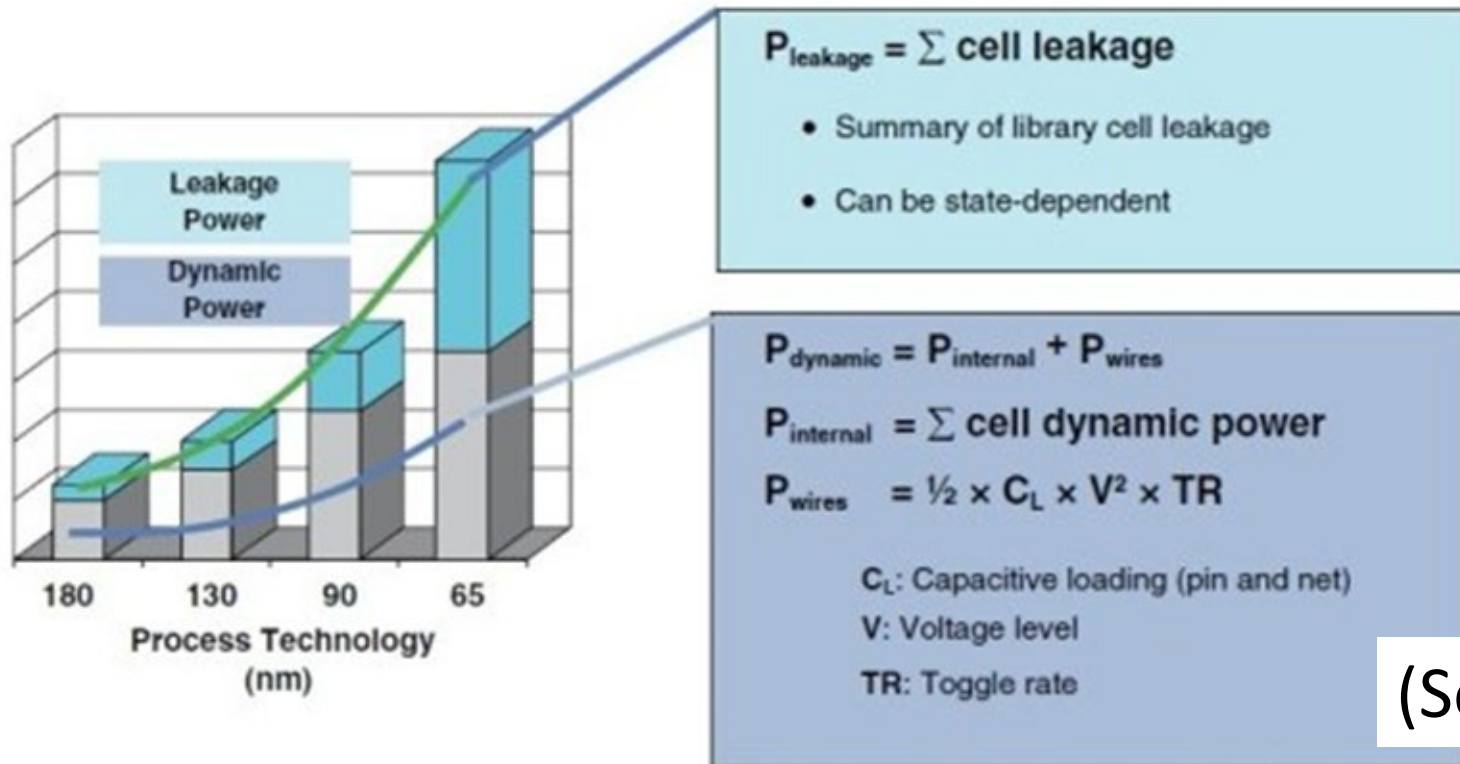5.3. Static power (1)

- Static power is consumed even when a chip is not switching.

$$P_{static} = (I_{sub} + I_{gate} + I_{junct} + I_{contention})V_{DD}$$



(Semiconductor Engineering)

5.3. Static power (2)

- Estimate the static power consumption.
 - 1.0 V 65 nm process (λ is 25 nm.)
 - 50M logic transistors (Average width: 12λ), 95 % of high- V_t , 5 % of low- V_t
 - 950M memory transistors (Average width: 4λ), all high- V_t
 - Total width of low- V_t transistors is $0.75 \times 10^6 \mu\text{m}$.
 - Total width of high- V_t transistors is $109.25 \times 10^6 \mu\text{m}$.
 - Subthreshold leakage currents: 100 nA/ μm for low- V_t , 10 nA/ μm for high- V_t
 - Gate leakage current: 5 nA/ μm
 - The answer is 859 mW.

5.3. Static power (3)

- Subthreshold leakage (for $V_{ds} > 50 \text{ mV}$)

$$I_{sub} = I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{DD}) - k_{\gamma} V_{sb}}{S}}$$

Transistor Type	High Speed Logic		Low Power Logic		High Voltage	
Options	High Performance (HP)	Standard Perf./ Power (SP)	Low Power (LP)	Ultra Low Power (ULP)	1.8 V	3.3 V
Vdd (Volt)	0.75 / 1	0.75 / 1	0.75 / 1	0.75/1.2	1.5/1.8/3.3	3.3 / >5
Gate Pitch (nm)	90	90	90	108	min. 180	min. 450
Lgate (nm)	30	34	34	40	min. 80	min. 280
N/PMOS Idsat/Ioff (mA/um)	1.08/ 0.91 @ 0.75 V, 100 nA/um	0.71 / 0.59 @ 0.75 V, 1 nA/um	0.41 / 0.37 @ 0.75 V 30 pA/um	0.35 / 0.33 @ 0.75 V 15 pA/um	0.92 / 0.8 @ 1.8 V 10 pA/um	1.0 / 0.85 @ 3.3 V 10 pA/um

(Intel's 2012 IEDM abstract)

5.3. Static power (4)

- Stack effect

$$I_{sub} = I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{DD}) - k_{\gamma} V_{sb}}{S}}$$

- N1 current

$$I_{sub} = I_{off} 10^{\frac{\eta(V_x - V_{DD})}{S}}$$

- N2 current

$$I_{sub} = I_{off} 10^{\frac{-V_x + \eta(V_{DD} - V_x - V_{DD}) - k_{\gamma} V_x}{S}}$$

- Then, with $V_x = \frac{\eta}{1+2\eta+k_{\gamma}} V_{DD}$,

$$I_{sub} = I_{off} 10^{\frac{-\eta V_{DD}}{S} \left(\frac{1+\eta+k_{\gamma}}{1+2\eta+k_{\gamma}} \right)}$$


 


Fig. 5.20

 5.3. Static power (5)



- Gate leakage
 - Various physical mechanisms
 - It is an extremely strong function of the dielectric thickness.
 - It also depends on the voltage across the gate.



Measured I_g - V_g characteristics
(Ho et al., EDL, vol. 18, pp. 209-211)

  5.3. Static power (6)

- High-k metal gate
 - Compare two technologies.



(Intel)

5.3. Static power (7)

- NAND3 leakage example (Leakage current in nA)

Input State (ABC)	I_{sub}	I_{gate}	I_{total}	V_x	V_z
000	0.4	0	0.4	stack effect	stack effect
001	0.7	0	0.7	stack effect	$V_{\text{DD}} - V_t$
010	0.7	1.3	2.0	intermediate	intermediate
011	3.8	0	3.8	$V_{\text{DD}} - V_t$	$V_{\text{DD}} - V_t$
100	0.7	6.3	7.0	0	stack effect
101	3.8	6.3	10.1	0	$V_{\text{DD}} - V_t$
110	5.6	12.6	18.2	0	0
111	28	18.9	46.9	0	0

Table 5.2

 


Fig. 5.23

5.3. Static power (8)

- Power gating
 - Turn OFF power to block when they are idle.
 - Use virtual V_{DD} (V_{DDV})
 - Gate outputs to prevent invalid logic level to next block

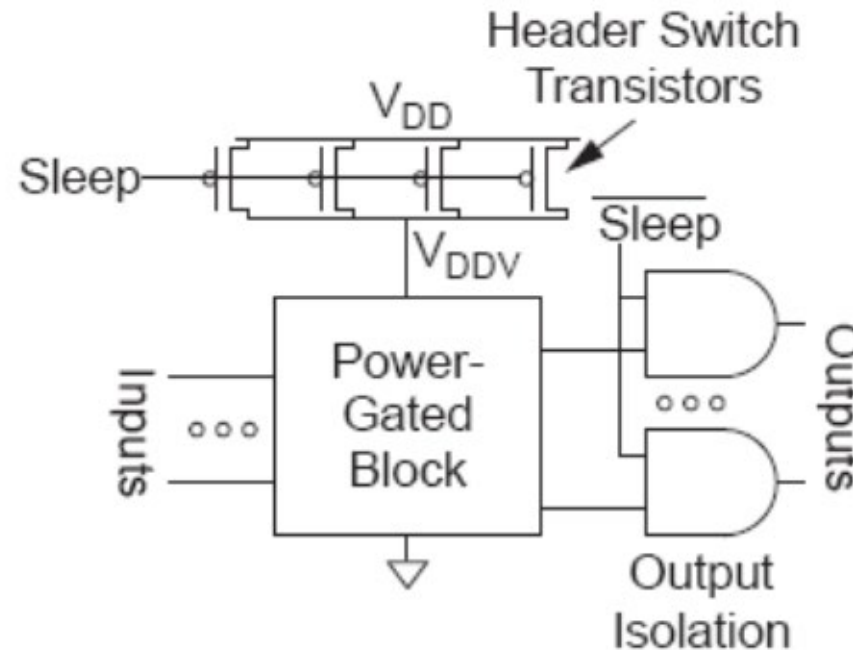


Fig. 5.24

Thank you!