

Digital Integrated Circuit

Lecture 20 Circuit Simulation

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Laboratory
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Review of Previous Lecture

Lecture 19

- Cu wire
 - Cu is a difficult material, however, we have managed to adopt it in the mass production.
- Wire capacitance
 - We need
 - Low-k material is desirable.
- Long wire
 - It significantly contributes to the delay.
 - Also, the energy consumption

8.1 Introduction

8.1. Introduction (1)


- **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis
 - Developed in 1970's at UC Berkeley
 - Many commercial versions are available. (For example, HSPICE)
- Initially, written in FORTRAN for punch-card machines
 - Circuit elements are called cards.
 - Complete description is called a SPICE deck.



Larry Nagel, the main author of SPICE (Google Images)

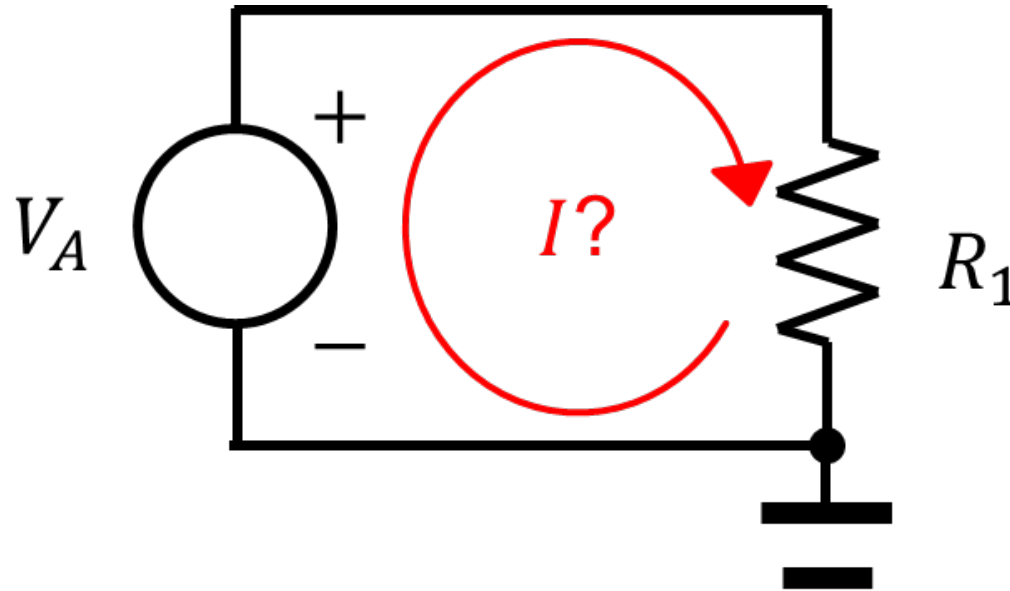8.1. Introduction (2)


- Consider a simple problem.
 - What is the current?



- Of course, you can easily answer that $I = \frac{V_A}{R_1}$.
 - But, how can we teach our computer to solve this problem?

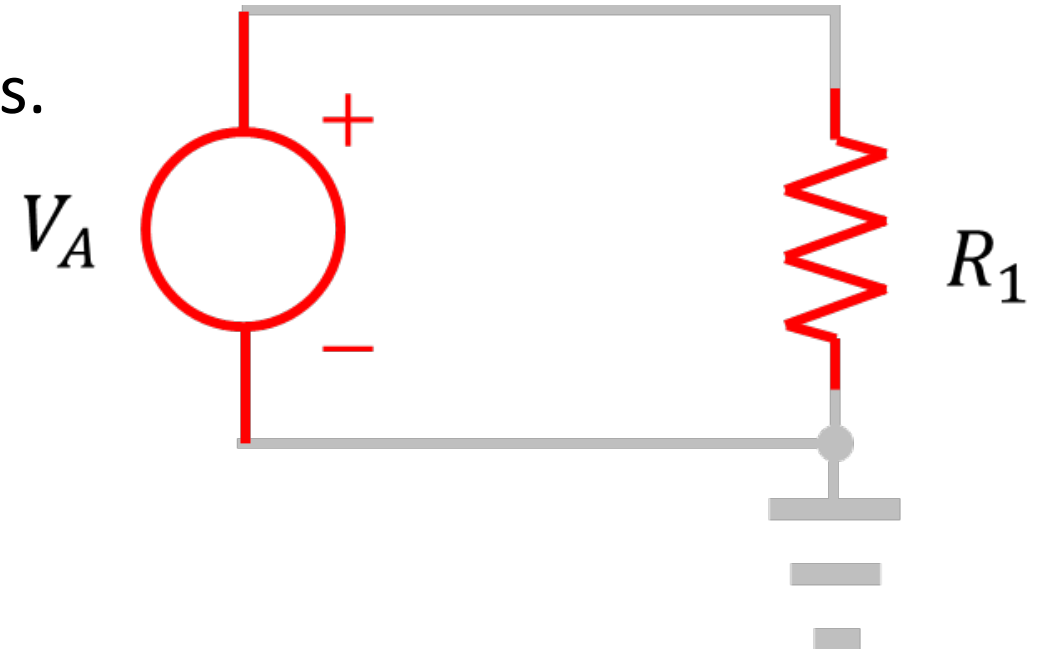
8.1. Introduction (3)

- Elements: Resistors, capacitors, etc
 - A circuit is made by connecting the elements.
 - They can have multiple terminals.
 - A resistor has two terminals.
 - A diode has two terminals.
 - A MOSFET has three (or four) terminals.



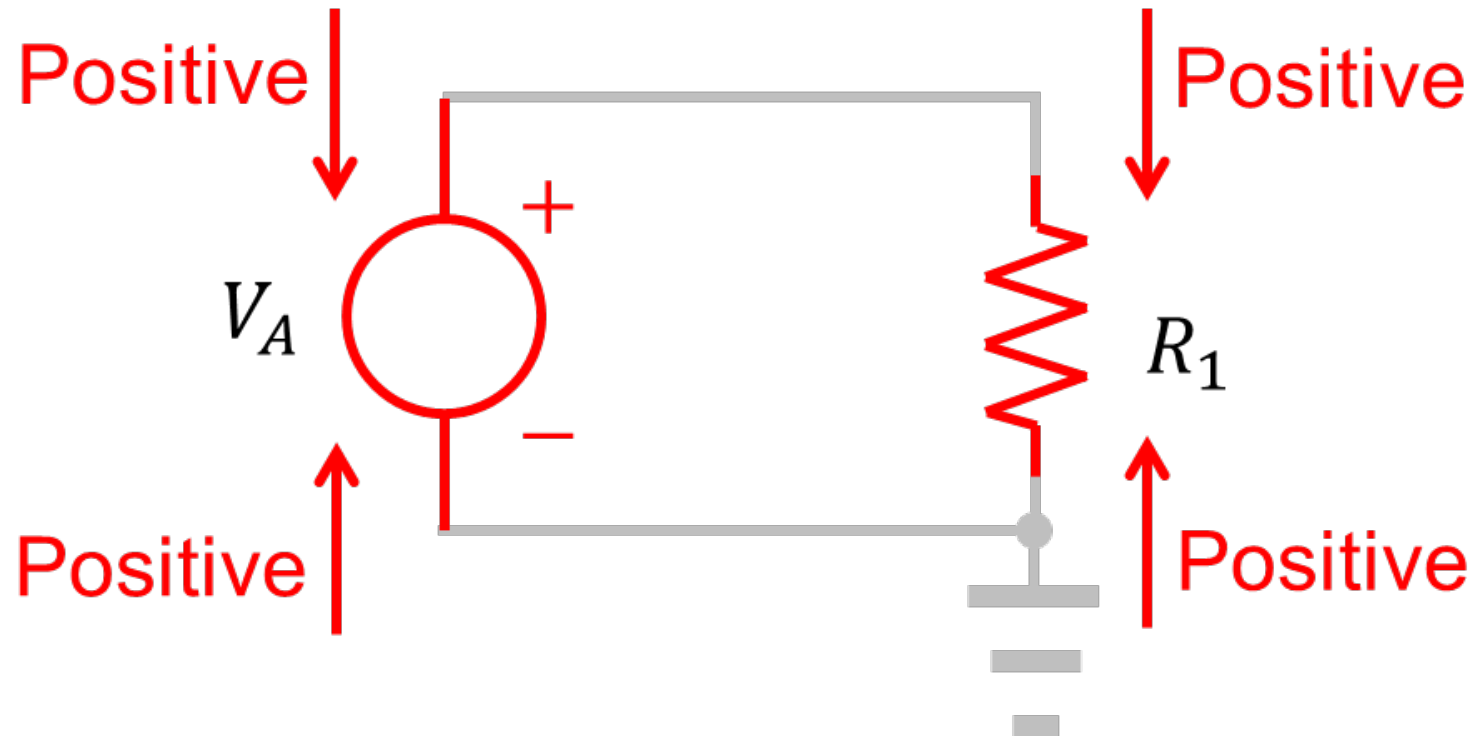
8.1. Introduction (4)

- Terminal current
 - Conventionally, an in-coming current is regarded as a positive one.



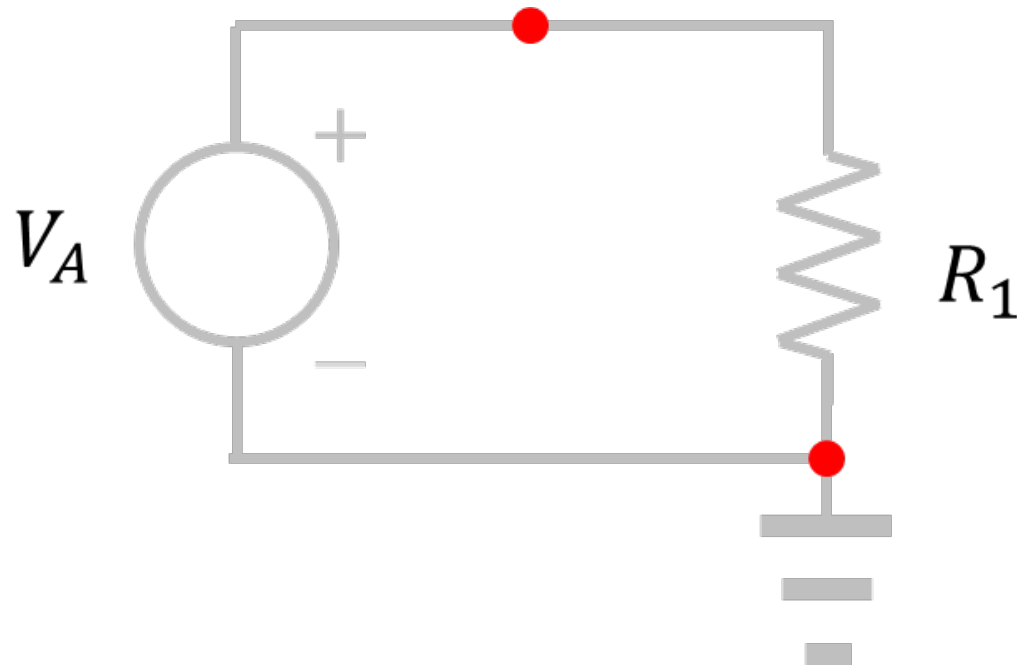8.1. Introduction (5)

- Node: A point to which multiple terminals are tied.
 - Usually, a dot is used to represent a node.
 - There is a special node, GND.




8.1. Introduction (6)

- How can we describe a circuit?
 - Of course, we can draw a circuit schematic. What else?
 - A netlist for this circuit reads:

```
va out 0 1.0
```

```
r1 out 0 1000
```

$va=1.0V$

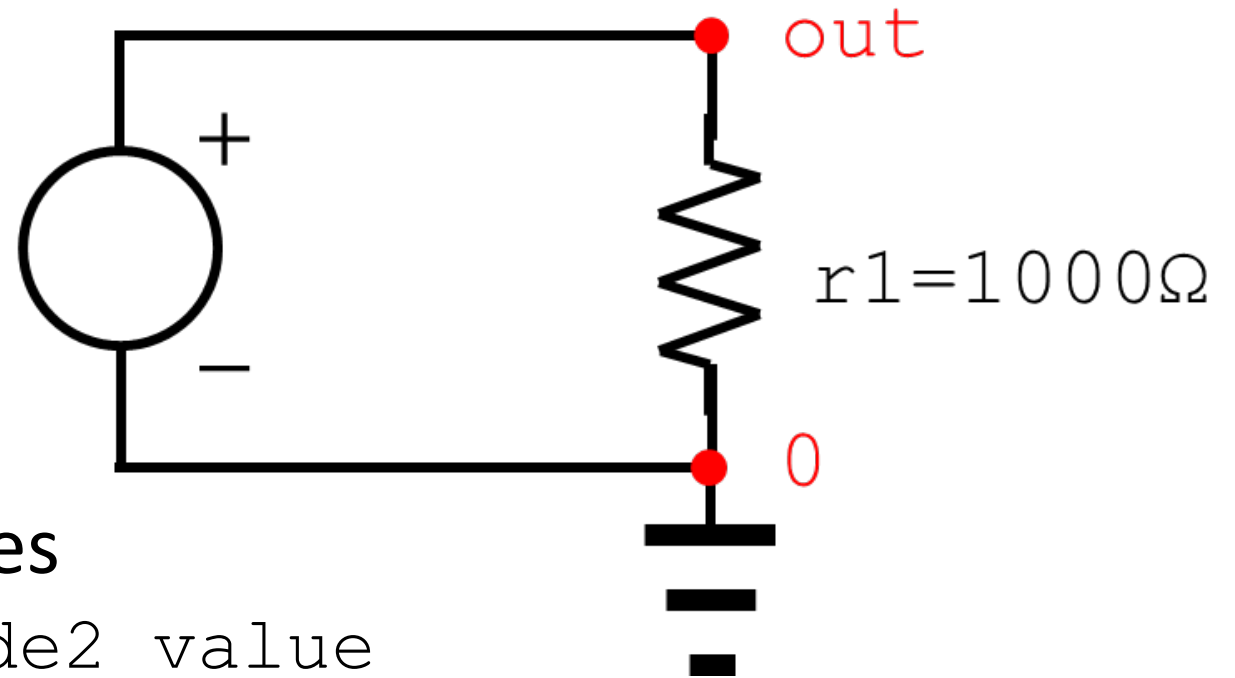

- Format for two-terminal devices

```
elementlabel1 node1 node2 value
```


8.1. Introduction (7)

- A netlist for this circuit reads:

```
c1 in out 5e-12
```


```
r1 out 0 2e6
```

```
vin in 0 1.5
```

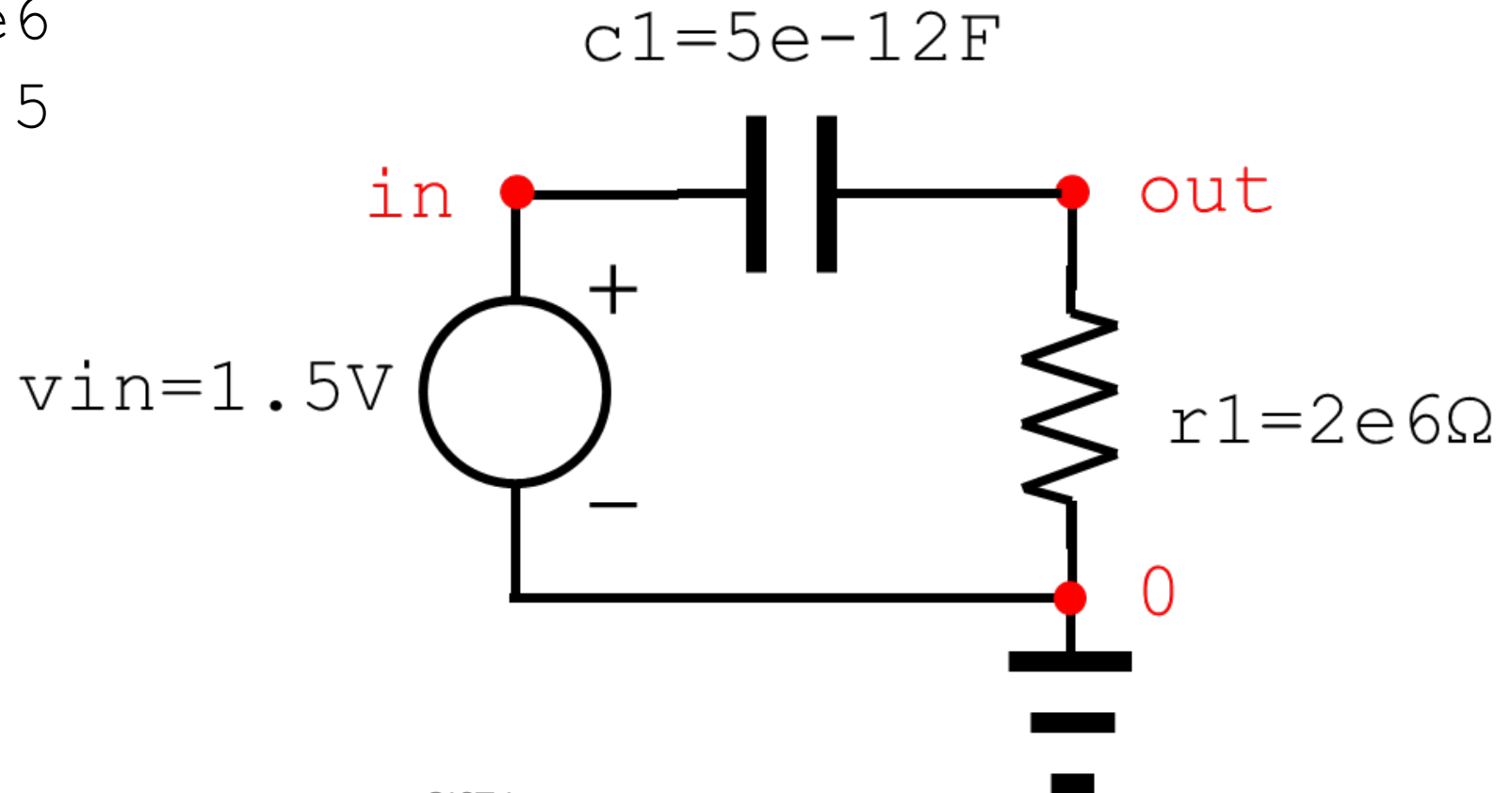

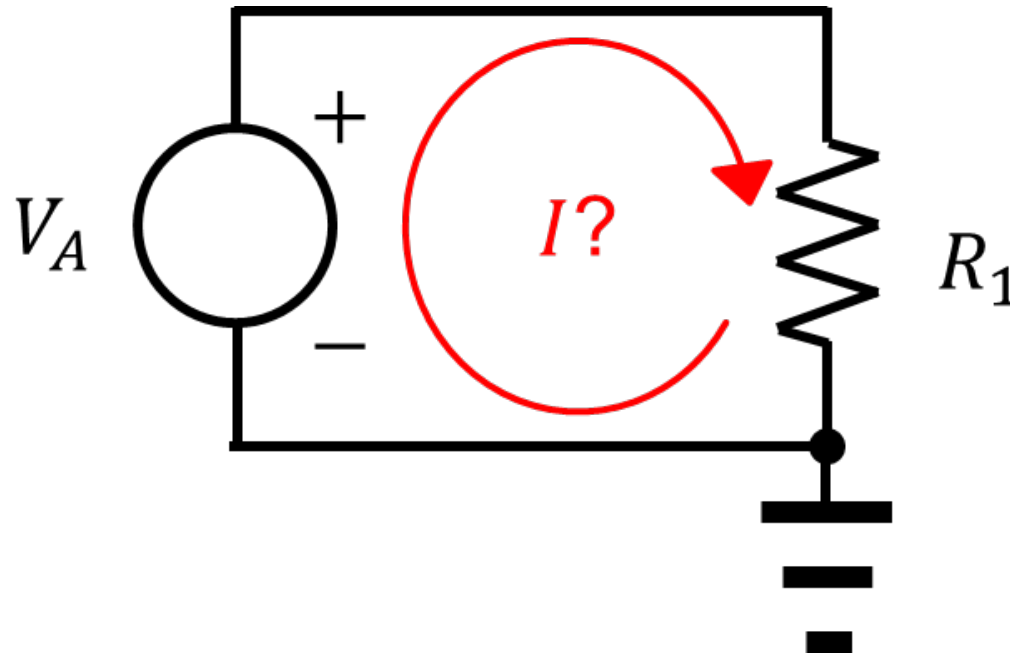8.1. Introduction (8)

- Solve a simple problem by a numerical means.
 - Identifying the governing equation



8.1. Introduction (9)

- Our simple problem

- We have only one node. Apply the KCL:

$$I_{va} + I_{r1} = 0 \quad \text{KCL}$$


- Two equations from elements:

Voltage source

$$V(out) - 0.0 = 1.0$$

Resistor

$$I_{r1} = \frac{V(out)}{1000}$$

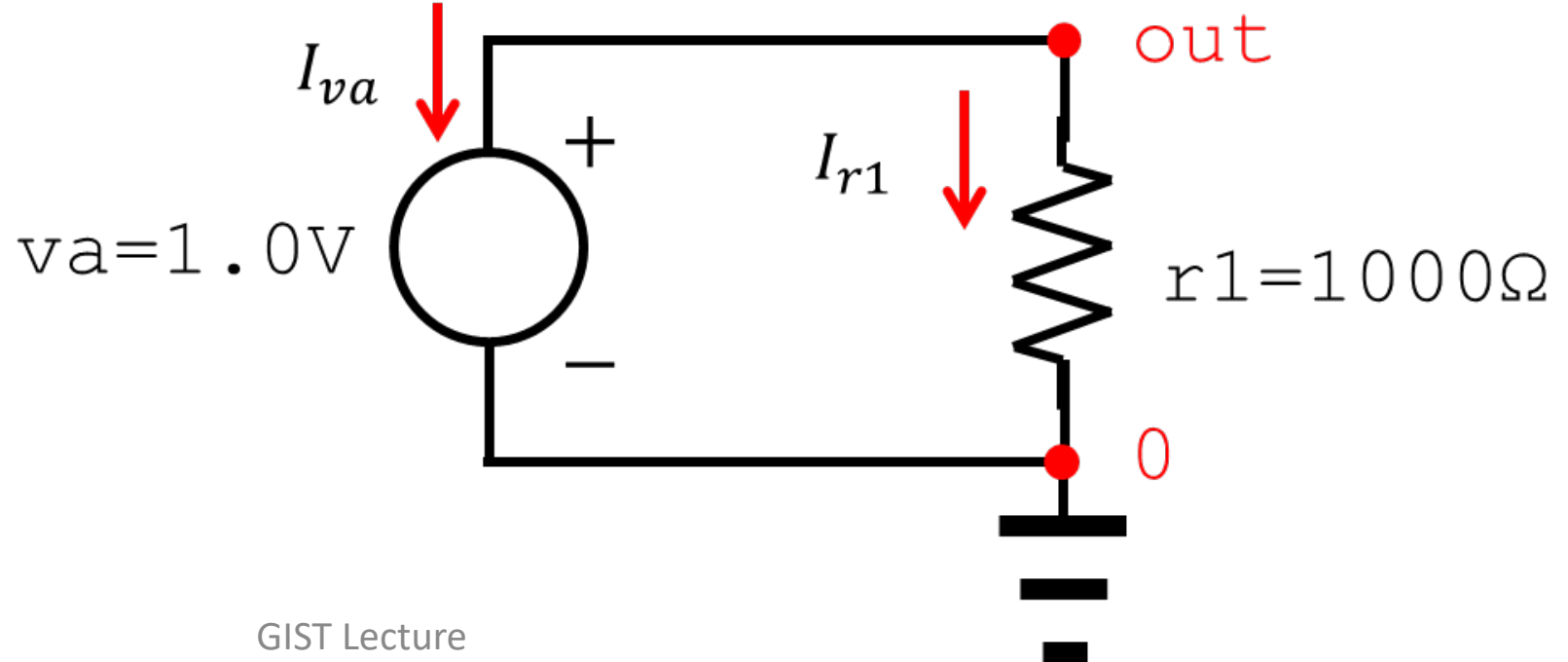

8.2 SPICE Tutorial

8.2. SPICE tutorial (1)

- Meaning of characters

| Letter | Unit | Magnitude |
|--------|-------|------------|
| a | atto | 10^{-18} |
| f | femto | 10^{-15} |
| p | pico | 10^{-12} |
| n | nano | 10^{-9} |
| u | micro | 10^{-6} |
| m | milli | 10^{-3} |
| k | kilo | 10^3 |
| x | mega | 10^6 |
| g | giga | 10^9 |

Table 8.2

| Letter | Element |
|--------|-----------------------------------|
| R | Resistor |
| C | Capacitor |
| L | Inductor |
| K | Mutual Inductor |
| V | Independent voltage source |
| I | Independent current source |
| M | MOSFET |
| D | Diode |
| Q | Bipolar transistor |
| W | Lossy transmission line |
| X | Subcircuit |
| E | Voltage-controlled voltage source |
| G | Voltage-controlled current source |
| H | Current-controlled voltage source |
| F | Current-controlled current source |

Table 8.1

8.2. SPICE tutorial (2)

- An example of RC circuit

```
* rc.sp for SPICE3F5  
Vin in 0 pwl 0ps 0 100ps 0 150ps 1.0 1ns 1.0  
R1 in out 2k  
C1 out 0 100f  
.tran 20ps 1ns  
.plot tran v(in) v(out)  
.end
```

Piecewise linear

TSTEP

TSTOP

8.2. SPICE tutorial (3)

- M element for MOSFET
 - For NMOSFETs and PMOSFETs,

Mname drain gate source body type

+ W=<width> L=<length>

+ AS=<area source> AD = <area drain>

+ PS=<perimeter source> PD=<perimeter drain>

8.2. SPICE tutorial (4)

- An example of DC analysis

```
* mosiv.sp for SPICE3F5
```

```
.include models_1p2mu.sp
```

```
Vgs g 0 0
```

VSTOP

```
Vds d 0 0
```

```
M1 d g 0 0 NMOS W=2.4 L=1.2
```

VSTART

VINCR

```
.dc Vds 0 5.0 0.05 Vgs 0 5.0 1.0
```

```
.print dc V(g) I(Vds)
```

```
.end
```

8.2. SPICE tutorial (5)

- An example of inverter
 - It calculates the voltage transfer curve.

```
* inv.sp for SPICE3F5

.include models_1p2mu.sp

Vdd vdd 0 5.0
Vin a 0 0.0
M1 y a 0 0 NMOS W=2.4 L=1.2
M2 y a vdd vdd PMOS W=4.8 L=1.2

.dc Vin 0 5 0.01
.print dc V(a) V(y)
.end
```

Homework#5

- Due: AM08:00, November 21
- Problem#1
 - Run the RC circuit example. (If you don't have any SPICE, then install it. For example, SPICE3f5 is freely available. You may try any SPICE.)
 - Show the simulation result.

Thank you!