

# Digital Integrated Circuit

## Lecture 23 Combinational Circuit Design

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**

# Lecture 22

- Static CMOS
  - Any logical function can be implemented with NAND/NOR/NOT gates.
  - Compound gates
  - By sizing transistors,  $t_{pdf}$  and  $t_{pdr}$  can be affected. (But, a benefit always comes with a cost.)

## 9.2 Circuit Families

## 9.2. Circuit families (10)

- Pseudo-NMOS
  - The static load is built from a single PMOS that has its gate grounded. (It is always ON.)
  - Voltage transfer curve affected by  $P$ .
  - Static DC current...


 
 


Fig. 9.13(c)
 
## 9.2. Circuit families (11)

- Compare the inverter design. (PMOS is 4 times weaker than NMOS.)
  - In the (output) falling transition, the following inverter drives the same current with the unit inverter. (*Why?*)
  - Certainly, it is faster for the falling transition.
  - On the other hand, it is slower for the rising transition.



$$\begin{aligned}g_u &= 4/3 \\g_d &= 4/9 \\g_{avg} &= 8/9 \\p_u &= 6/3 \\p_d &= 6/9 \\p_{avg} &= 12/9\end{aligned}$$

## 9.2. Circuit families (12)

- Comments on ratioed circuits
  - They reduce the input capacitance by replacing the PMOS transistors connected to the input with a single resistive pullup.
  - Drawbacks:
    - Slow rising transitions
    - Contention on the falling transitions
    - Static power dissipation
    - Nonzero  $V_{OL}$

## 9.2. Circuit families (13)

- Dynamic gates use a clocked PMOS pullup.
- Two modes: *precharge* and *evaluate*

 


Fig. 9.21

 


Fig. 9.22



## 9.2. Circuit families (14)

- What if pulldown network is ON during precharge?
- An extra clocked evaluation transistor can be added to avoid contention.



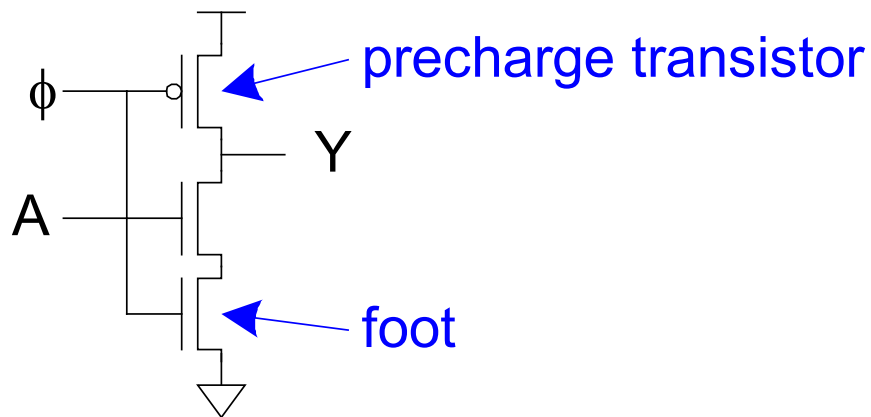


Fig. 9.23

 

footed

 


unfooted

Fig. 9.24

# 9.2. Circuit families (15)

- Catalog of dynamic gates

 

## 9.2. Circuit families (16)

- Dynamic gates require *monotonically rising* inputs during evaluation.

–  $0 \rightarrow 0, 0 \rightarrow 1, 1 \rightarrow 1$ . But not  $1 \rightarrow 0$


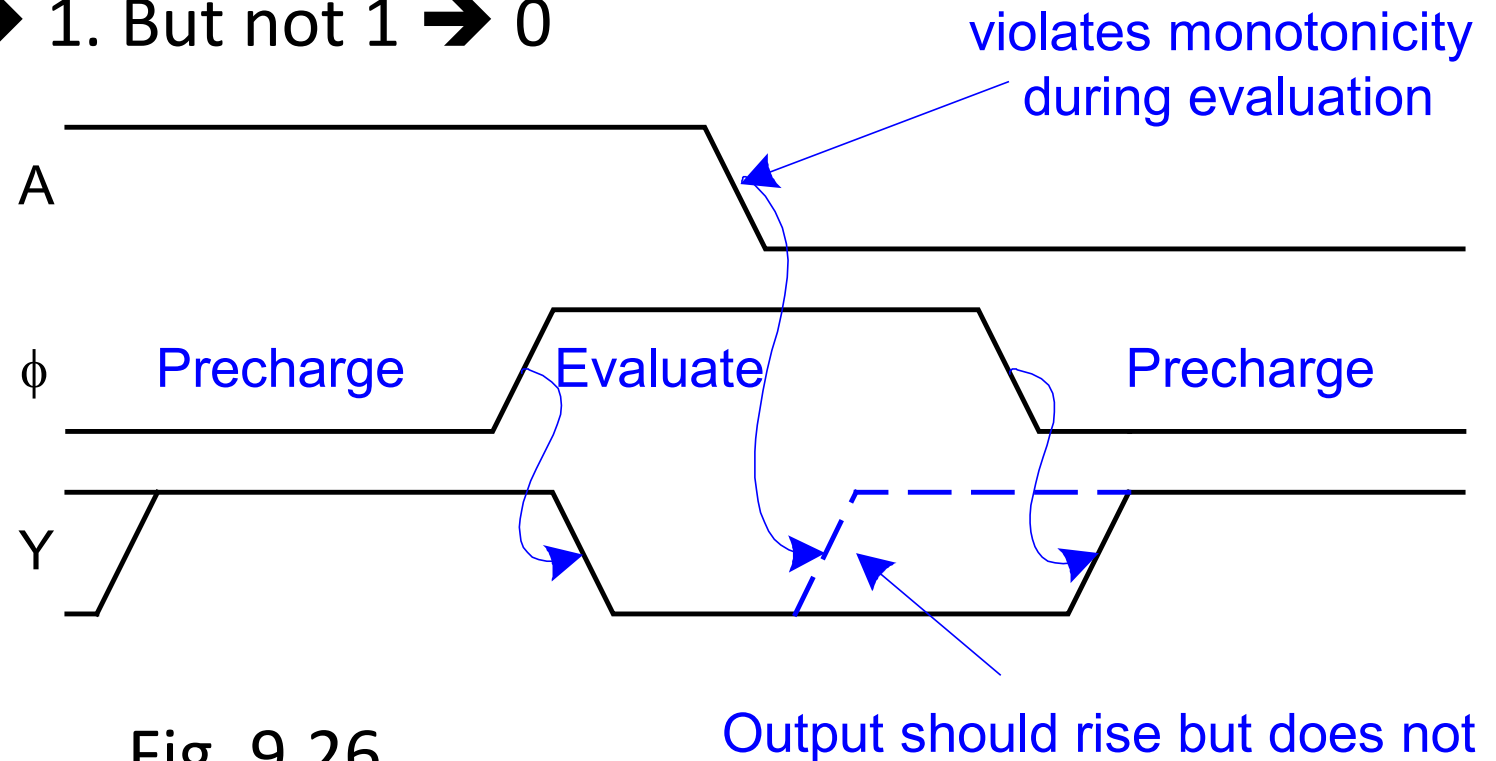
 
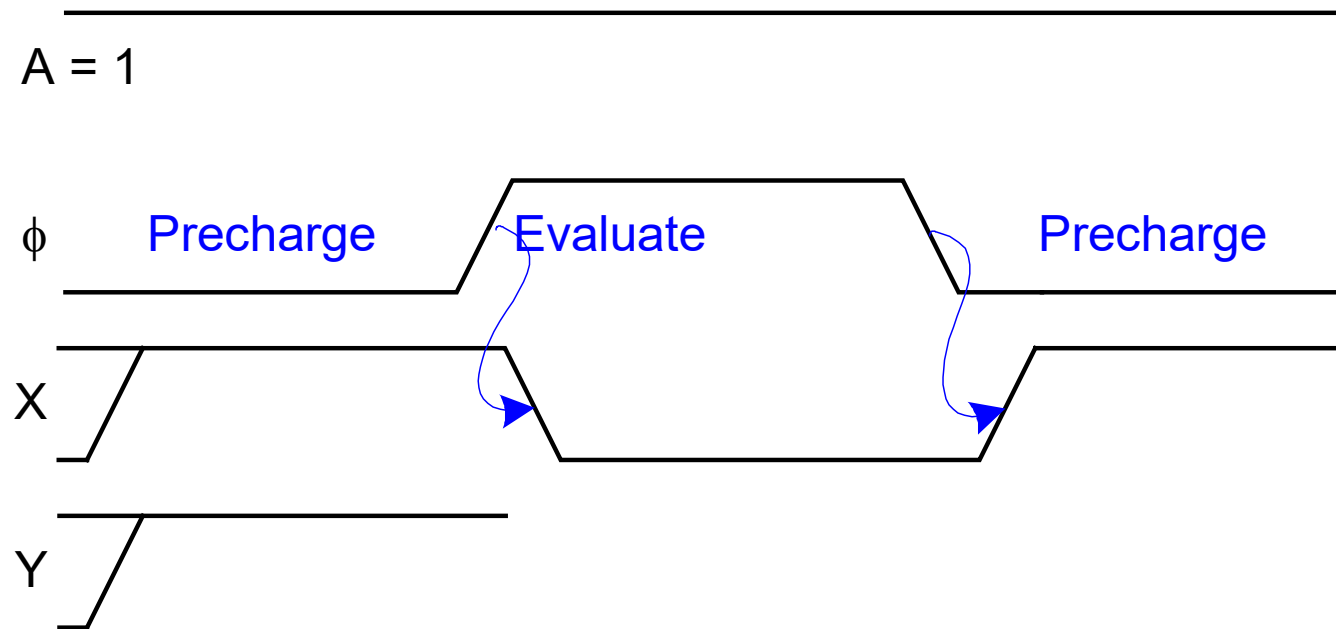


Fig. 9.26
 
## 9.2. Circuit families (17)

- But, dynamic gates produce monotonically falling outputs during evaluation.
  - Dynamic gates sharing the same clock cannot be directly connected.



Draw it!

## 9.2. Circuit families (18)

- Place a static CMOS inverter between dynamic gates.
  - The dynamic-static pair is called a *domino* gate.
  - The dynamic output is monotonically falling during evaluation.


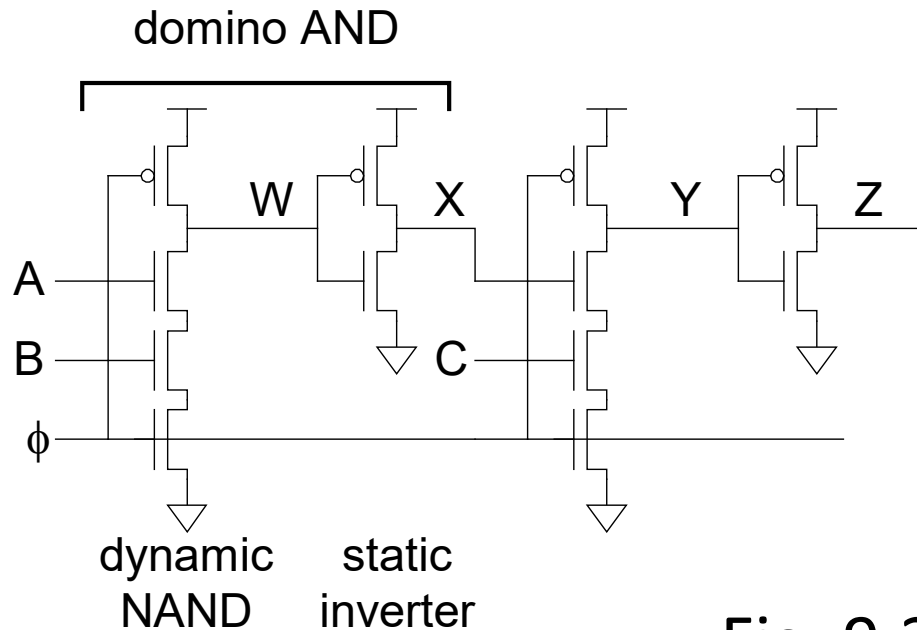
 


Fig. 9.28

 

## 9.2. Circuit families (19)

- Each domino gate triggers next one, like a string of dominos toppling over.
  - Precharge occurs in parallel, but evaluation occurs sequentially.
  - Thus, evaluation is more critical than precharge.
  - HI-skewed static stages can perform logic.

## 9.2. Circuit families (20)

- Compound domino
  - More complex inverting static CMOS gates such as NANDs or NORs in place of the inverter


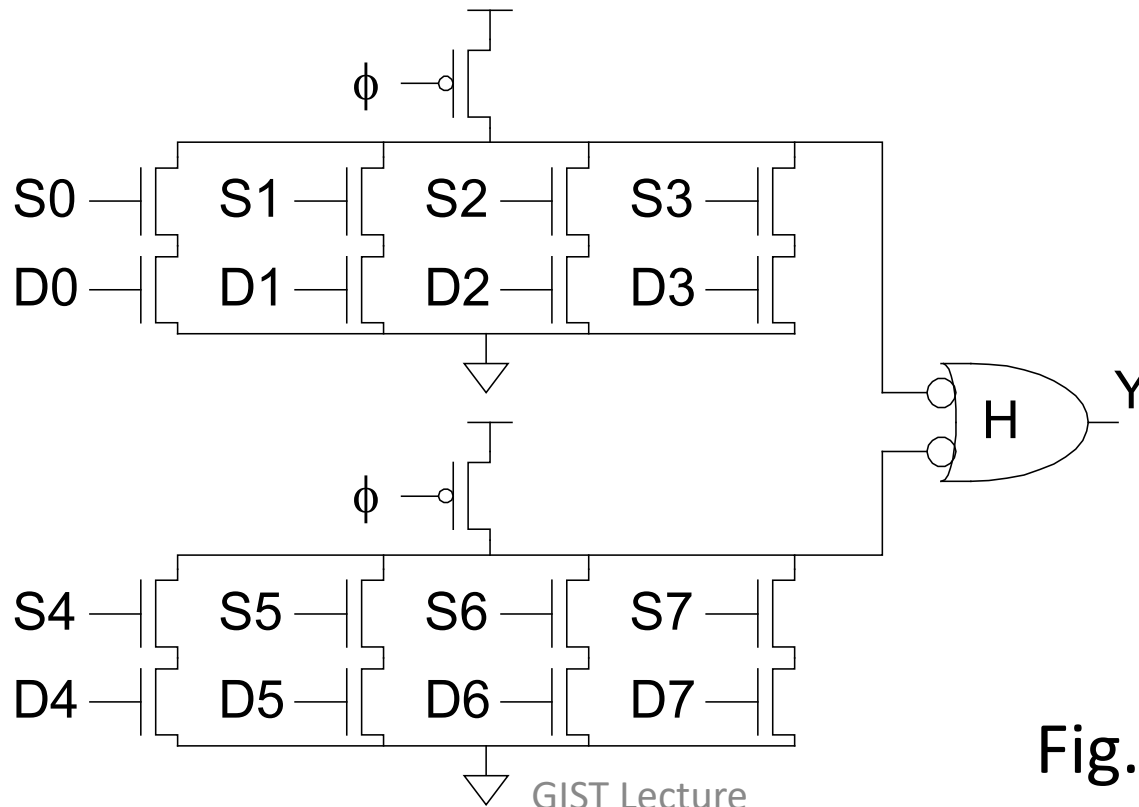


Fig. 9.29
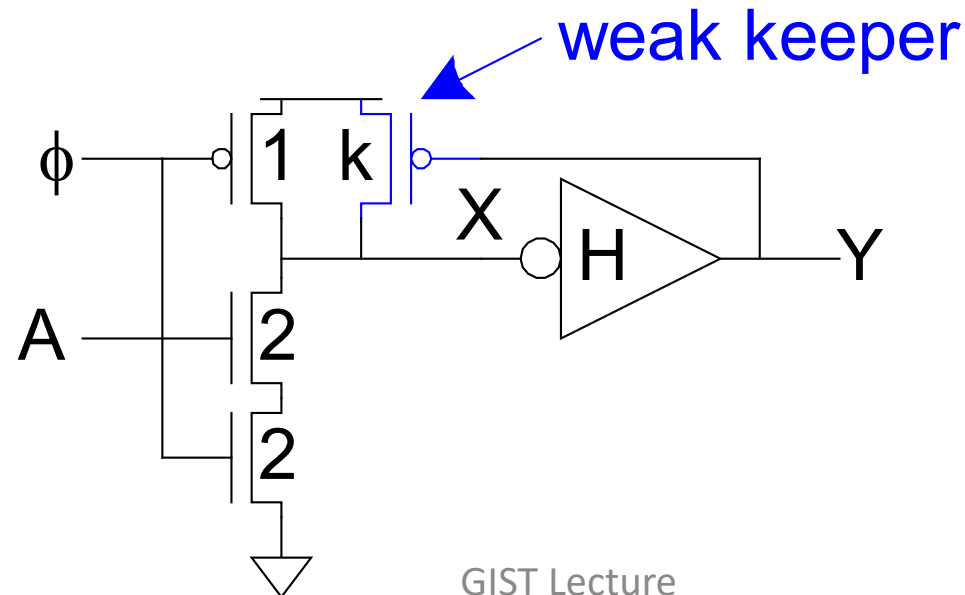
## 9.2. Circuit families (21)



- Dynamic node floats high during evaluation.
  - Transistors are leaky. (We have non-negligible  $I_{OFF}$ .)
  - Dynamic value will leak away over time.
- Use keeper to hold dynamic node.
  - Must be weak enough not to fight evaluation




  
## 9.2. Circuit families (22)

- Pass transistor circuits
  - Use pass transistors like switches to do logic
  - Example) 2-input multiplexer



# Thank you!