

# Digital Integrated Circuit

## Lecture 16 Power

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**

# Lecture 15

- Power

- Instantaneous power


$$P(t) = I(t)V(t)$$

- Switching power consumption

$$P_{switching} = \frac{CV_{DD}^2}{T} = CV_{DD}^2 f_{sw}$$

# Apple M2 CPU performance

- Performance-power graph

 

(Apple)

## **5.2 Dynamic Power**

## 5.2. Dynamic power (1)

- Estimate the switching power when operating at 1 GHz.
  - 1.0 V 65 nm process ( $\lambda$  is 25 nm.)
  - $C = 1 \text{ fF}/\mu\text{m}$  (gate) +  $0.8 \text{ fF}/\mu\text{m}$  (diffusion)
  - 50M logic transistors (Average width:  $12\lambda$ ), activity factor = 0.1
  - 950M memory transistors (Average width:  $4\lambda$ ), activity factor = 0.02
  - Each transistor has a capacitance of  $1.8 \text{ fF}/\mu\text{m}$ .
  - For logic transistors, the capacitance is 27 nF.
  - For memory transistors, the capacitance is 171 nF.
  - The answer is 6.1 W.

## 5.2. Dynamic power (2)

- Remember that

$$P_{switching} = \alpha C V_{DD}^2 f$$

- Try to minimize:
- Activity factor ( $\alpha$ )
- Capacitance ( $C$ )
- Supply voltage ( $V_{DD}^2$ )
- Frequency ( $f$ )

## 5.2. Dynamic power (3)

- Activity factor estimation

- Define  $P_i$  to be the probability that node  $i$  is 1. Also,  $\bar{P}_i = 1 - P_i$ .

- Then,

$$\alpha_i = \bar{P}_i P_i \quad \leftarrow \text{Assumption?}$$

- Completely random data has  $P_i = 0.5$  and  $\alpha = 0.25$ . (It is the maximum value of  $\bar{P}_i P_i$ .)

- Data is often not completely random.



## 5.2. Dynamic power (5)


- Switching probability
  - Activity factor of the output is  $\overline{P_Y} P_Y$ .

Gate	$P_Y$
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \overline{P_A} \overline{P_B}$
NAND2	$1 - P_A P_B$
NOR2	$\overline{P_A} \overline{P_B}$
XOR2	$P_A \overline{P_B} + \overline{P_A} P_B$

Table 5.1
 
## 5.2. Dynamic power (6)

- A 4-input AND
  - Two-level implementation
$$Y = \overline{\overline{AB}} + \overline{\overline{CD}} = \overline{\overline{AB}} \overline{\overline{CD}} = ABCD$$
  - Estimate the activity factor at each node if the inputs have  $P = 0.5$ .



## 5.2. Dynamic power (7)

- Capacitance
- Gate capacitance (In this text, “gate” is not a contact.)
  - Fewer stages of logic
  - Small gate sizes
- Wire capacitance
  - Good floorplanning to keep communicating blocks close to each other
  - Drive long wires with inverters or buffers rather than complex gates

## 5.2. Dynamic power (8)

- Voltage domains
  - Provide separate supplies to different blocks
  - Level converters required when crossing from low to high  $V_{DD}$  domains

 


Fig. 5.15

- Frequency
  - Dynamic power is directly proportional to frequency. A chip should not run faster than necessary.

# Thank you!