

# Digital Integrated Circuit

## Lecture 10 Delay



Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Laboratory  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# **Review of Previous Lecture**
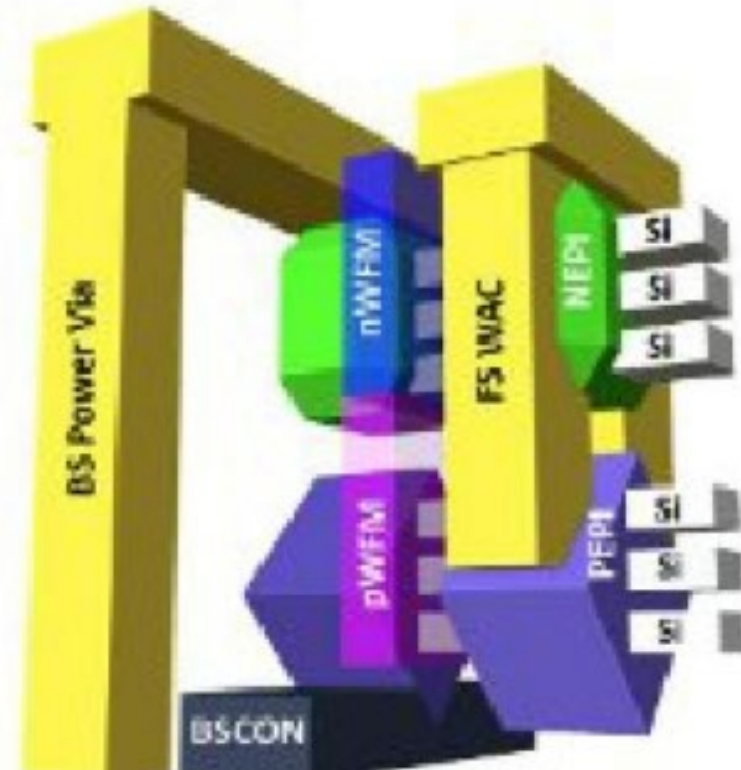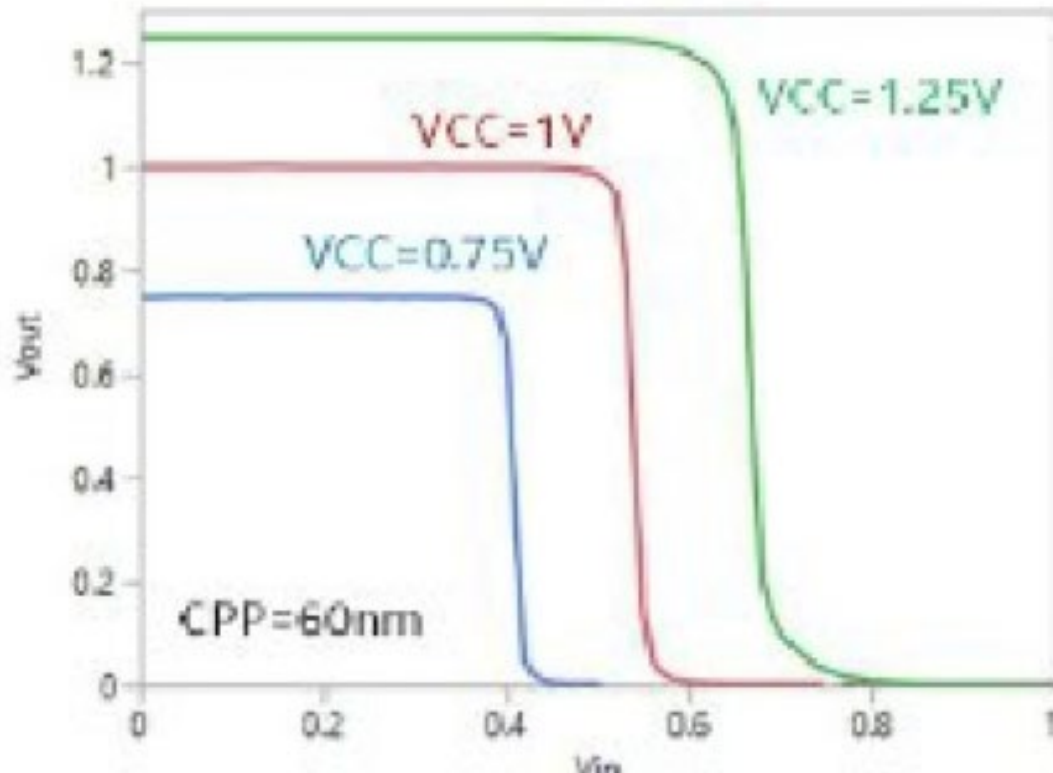
# Lecture 9

- CMOS inverter
  - Skewed due to the N/P mismatch



(Taken from IEDM 2023 press kit)

## 2.5 DC Transfer

## 2.5. DC transfer (9)

- Noise margin

- Two unity gain points
- Input voltage is  $V_{IL}$ .
- Input voltage is  $V_{IH}$ .

– In this case,

$$NL_L = V_{IL}$$

$$NL_H = V_{DD} - V_{IH}$$

 


Fig. 2.30

# Homework#3

- Due: AM08:00, October 10
- Problem#1
  - Calculate  $V_{IL}$  with the ideal IV characteristics. It can be found from a condition of  $\frac{dV_{out}}{dV_{in}} = -1$ . Neglect the channel length modulation.
  - Assume  $\mu_n C_{OX} \frac{W_n}{L_n} = \mu_p C_{OX} \frac{W_p}{L_p}$  and  $V_{tn} = -V_{tp}$  for simplicity.
  - Hint: The NMOSFET is in the saturation mode, while the PMOSFET in the linear mode.

# Homework#3

- Problem#2

- Using the solution of Problem#1, calculate  $V_{IL}$  when  $V_{DD}$  is 1.8 V and  $V_{tn}$  is 0.5 V.

# 4.1 Introduction



# 4.1. Introduction (1)

- Transient response

- DC analysis:  $V_{out}$  if  $V_{in}$  is a constant
- Transient analysis:  $V_{out}(t)$  if  $V_{in}(t)$  changes
- A set of differential equations should be solved.
- For a vector of state variable,  $\mathbf{x}$ ,

$$\frac{d}{dt}(\mathbf{C} \mathbf{x}) + G(\mathbf{x}) = \mathbf{b}$$

- Input is usually considered to be a step or ramp. (From 0 to  $V_{DD}$  or vice versa)

# 4.1. Introduction (2)

- Definitions

- $t_{pdr}$ : *rising propagation delay*

From input to rising output crossing  $V_{DD}/2$

- $t_{pdf}$ : *falling propagation delay*

From input to falling output crossing  $V_{DD}/2$

- $t_{pd}$ : *average propagation delay*

$$t_{pd} = (t_{pdr} + t_{pdf})/2$$

- $t_r$ : *rise time*

From output crossing  $0.2 V_{DD}$  to  $0.8 V_{DD}$

- $t_f$ : *fall time*

From output crossing  $0.8 V_{DD}$  to  $0.2 V_{DD}$


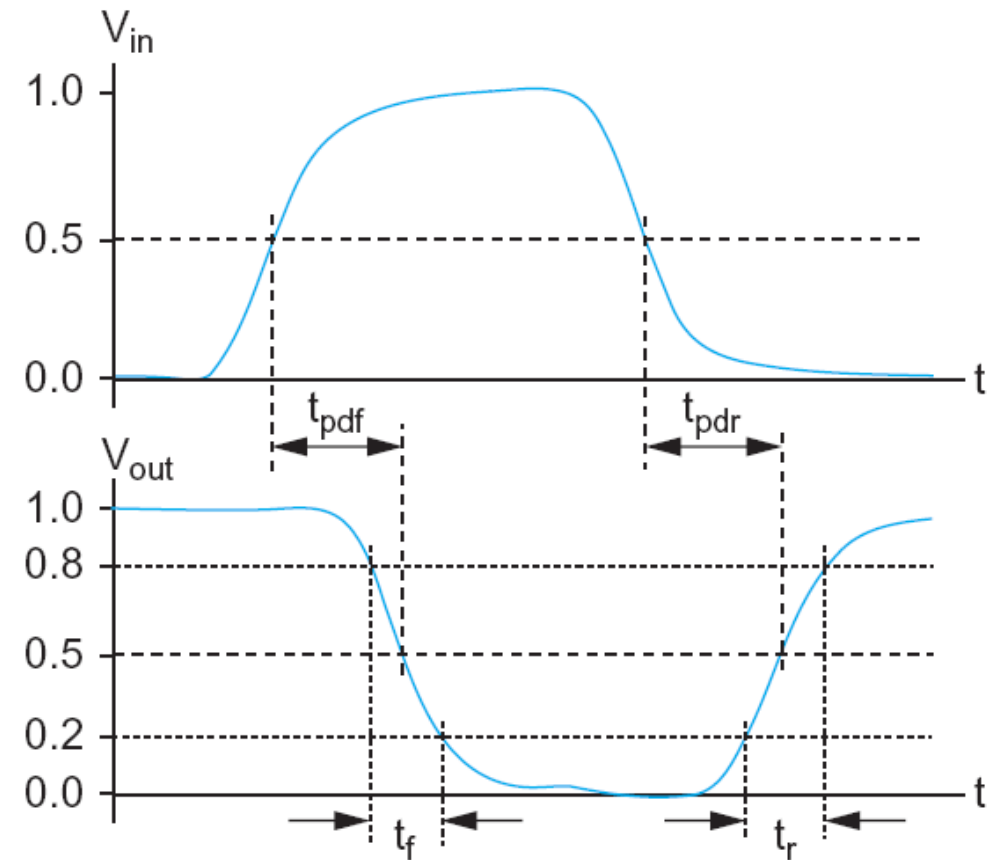


Fig. 4.1

## 4.2. Transient response (1)

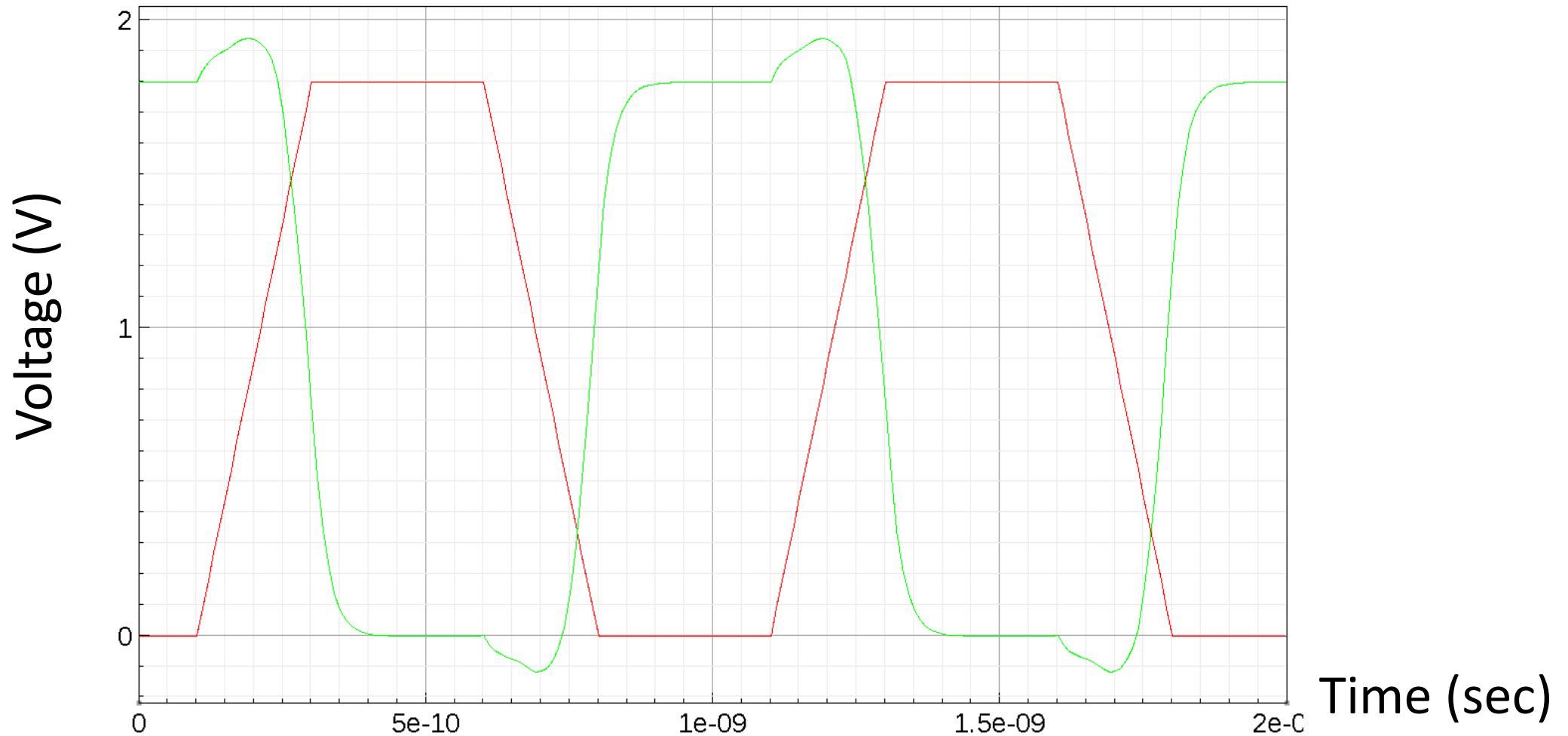- Example of an inverter ( $V_{DD} = 1.8$  V)



## 4.2. Transient response (2)

- Consider a falling edge of an inverter.
  - Initially,  $V_{in} = 0$  V and  $V_{out} = V_{DD}$ .
  - With a sudden turn-on,  $V_{in} = V_{DD}$ . The PMOSFET is turned off.

$$C_{out} \frac{dV_{out}}{dt} = -I_{dn}$$

- For saturation,

$$I_{dn} = \frac{\beta}{2} (V_{DD} - V_t)^2 \quad \leftarrow \text{It is a constant.}$$

- For linear,

$$I_{dn} = \beta \left( V_{DD} - V_t - \frac{V_{out}}{2} \right) V_{out}$$

# Homework#3

- Problem#3

- Draw the response of the inverter to a step input. (LOW→HIGH) For the NMOSFET,  $W$  is 1  $\mu\text{m}$  and  $L$  is 50 nm. Its oxide thickness is 10.5 Å and the mobility is 80  $\text{cm}^2/\text{V sec}$ . The output capacitance is 20 fF.  $V_{DD}$  is 1.0 V and  $V_{tn}$  is 0.3 V.
- (You may use the computer to draw the curve accurately.)

- Problem#4

- In Problem#3, estimate the falling propagation delay.

# Thank you!